

BLM5207
Computer Organization

Prof. Dr. Nizamettin AYDIN
naydin@yildiz.edu.tr
<http://www3.yildiz.edu.tr/~naydin>

Digital Logic

1

1

Introduction

- In the latter part of the nineteenth century, George Boole incensed philosophers and mathematicians alike when he suggested that logical thought could be represented through mathematical equations.
 - How dare anyone suggest that human thought could be encapsulated and manipulated like an algebraic formula?
- Computers, as we know them today, are implementations of Boole's Laws of Thought.
 - John Atanasoff and Claude Shannon were among the first to see this connection

2

2

Introduction

- In the middle of the twentieth century, computers were commonly known as **thinking machines** and **electronic brains**.
 - Many people were fearful of them.
- Nowadays, we rarely ponder the relationship between electronic digital computers and human logic.
- Computers are accepted as part of our lives.
 - Many people, however, are still fearful of them.
- In this lecture, you will learn the simplicity that constitutes the essence of the machine.

3

3

Boolean Algebra

- Boolean algebra is a mathematical system for the manipulation of variables that can have one of two values.
 - In formal logic, these values are **true** and **false**.
 - In digital systems, these values are **on** and **off**, **1** and **0**, or **high** and **low**.
- Boolean expressions are created by performing operations on Boolean variables.
 - Common Boolean operators include **AND**, **OR**, and **NOT**.

4

4

Boolean Algebra

- A Boolean operator can be completely described using a **truth table**.
 - The truth table for the Boolean operators **AND**, **OR**, and **NOT** are shown at the right.
 - The **AND** operator is also known as a Boolean product.
 - The **OR** operator is the Boolean sum.
 - The **NOT** operation is most often designated by an overbar.
 - It is sometimes indicated by a prime mark (') or an "elbow" (⌋).

X AND Y		
X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT X	
X	\bar{X}
0	1
1	0

5

5

Boolean Algebra

- A Boolean function has:
 - At least one Boolean variable,
 - At least one Boolean operator, and
 - At least one input from the set {0,1}.
- It produces an output that is also a member of the set {0,1}.
 - Now you know why the binary numbering system is so handy in digital systems.

6

6

Boolean Algebra

- The truth table for the Boolean function:

$$F(x, y, z) = x\bar{z} + y$$

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

- To make evaluation of the Boolean function easier, the truth table contains extra (shaded) columns to hold evaluations of subparts of the function.

7

Boolean Algebra

- As with common arithmetic, Boolean operations have rules of precedence.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

- The NOT operator has highest priority, followed by AND and then OR.

- This is how we chose the (shaded) function subparts in our table.

8

Boolean Algebra

- Digital computers contain circuits that implement Boolean functions.
- The simpler that we can make a Boolean function, the smaller the circuit that will result.
 - Simpler circuits are cheaper to build, consume less power, and run faster than complex circuits.
- With this in mind, we always want to reduce our Boolean functions to their simplest form.
- There are a number of Boolean identities that help us to do this.

9

Boolean Algebra

- Most Boolean identities have an AND (product) form as well as an OR (sum) form.
- First group is rather intuitive:

Identity Name	AND Form	OR Form
Identity Law	$1x = x$	$0 + x = x$
Null Law	$0x = 0$	$1 + x = 1$
Idempotent Law	$xx = x$	$x + x = x$
Inverse Law	$x\bar{x} = 0$	$x + \bar{x} = 1$

10

Boolean Algebra

- Second group of Boolean identities:

Identity Name	AND Form	OR Form
Commutative Law	$xy = yx$	$x+y = y+x$
Associative Law	$(xy)z = x(yz)$	$(x+y)+z = x+(y+z)$
Distributive Law	$x+yz = (x+y)(x+z)$	$x(y+z) = xy+xz$

- Third group of Boolean identities:

Identity Name	AND Form	OR Form
Absorption Law	$x(x+y) = x$	$x + xy = x$
DeMorgan's Law	$\overline{(xy)} = \bar{x} + \bar{y}$	$\overline{(x+y)} = \bar{x}\bar{y}$
Double Complement Law	$\overline{(\bar{x})} = x$	

11

Boolean Algebra

- We can use Boolean identities to simplify the function $F(x, y, z) = (x + y)(x + \bar{y})(x\bar{z})$ as follows:

$(x + y)(x + \bar{y})(x\bar{z})$	Idempotent Law (Rewriting)
$(x + y)(x + \bar{y})(\bar{x}\bar{z})$	DeMorgan's Law
$(xx + x\bar{y} + xy + y\bar{y})(\bar{x}\bar{z})$	Distributive Law
$((x + y\bar{y}) + x(y + \bar{y}))(\bar{x}\bar{z})$	Commutative & Distributive Laws
$(x + 0) + x(1)(\bar{x}\bar{z})$	Inverse Law
$x(\bar{x}\bar{z})$	Idempotent Law
$x\bar{x} + x\bar{z}$	Distributive Law
$0 + x\bar{z}$	Inverse Law
$x\bar{z}$	Idempotent Law

12

11

12

Boolean Algebra

- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly.
- DeMorgan's law provides an easy way of finding the complement of a Boolean function.
- Recall DeMorgan's law states:

$$\overline{(xy)} = \bar{x} + \bar{y} \quad \text{and} \quad \overline{(x+y)} = \bar{x}\bar{y}$$

13

13

Boolean Algebra

- DeMorgan's law can be extended to any number of variables.
- Replace each variable by its complement and change all **ANDs** to **ORs** and all **ORs** to **ANDs**.
- Thus, we find the complement of:

$$F(x, y, z) = (xy) + (\bar{x}z) + (y\bar{z})$$

as:

$$\begin{aligned} \overline{F(x, y, z)} &= \overline{(xy) + (\bar{x}z) + (y\bar{z})} \\ &= \overline{(xy)} \overline{(\bar{x}z)} \overline{(y\bar{z})} \\ &= (\bar{x} + \bar{y})(x + \bar{z})(\bar{y} + z) \end{aligned}$$

14

14

Boolean Algebra

- Through our exercises in simplifying Boolean expressions, we see that there are numerous ways of stating the same Boolean expression.
 - These **synonymous forms** are **logically equivalent**.
 - **Logically equivalent expressions have identical truth tables.**
- In order to eliminate as much confusion as possible, designers express Boolean functions in **standardized** or **canonical form**.

15

15

Boolean Algebra

- There are two canonical forms for Boolean expressions:
 - **sum-of-products**
 - **product-of-sums**
 - Recall the **Boolean product** is the **AND** operation and the **Boolean sum** is the **OR** operation.
- In the sum-of-products form, **ANDed** variables are **ORed** together.
 - For example: $F(x, y, z) = xy + xz + yz$
- In the product-of-sums form, **ORed** variables are **ANDed** together:
 - For example: $F(x, y, z) = (x+y)(x+z)(y+z)$

16

16

Boolean Algebra

- It is easy to convert a function to sum-of-products form using its truth table.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- We are interested in the values of the variables that make the function true (=1).
- Using the truth table, we list the values of the variables that result in a true function value.
- Each group of variables is then **ORed** together.

17

17

Boolean Algebra

- The sum-of-products form for our function is:

$$F(x, y, z) = \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- We note that this function is not in simplest terms.
- Our aim is only to rewrite our function in canonical sum-of-products form.

18

18

Logic Gates


- We have looked at Boolean functions in abstract terms.
- In this section, we see that Boolean functions are implemented in **digital computer circuits** called **gates**.
- A **gate** is an electronic device that produces a result based on two or more input values.
 - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit.
 - Integrated circuits contain collections of gates suited to a particular purpose.

19

19

Logic Gates

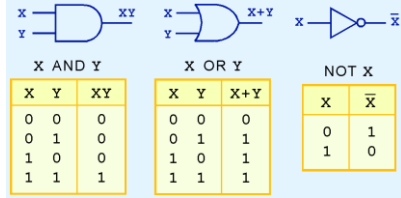- The three simplest gates are the AND, OR, and NOT gates.




- They correspond directly to their respective Boolean operations, as you can see by their truth tables.

20

20

Logic Gates

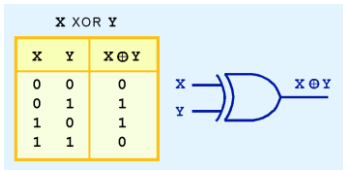- Another very useful gate is the exclusive OR (XOR) gate.
 - The output of the XOR operation is true only when the values of the inputs differ.




- Note the special symbol \oplus for the XOR operation.

21

21

Logic Gates

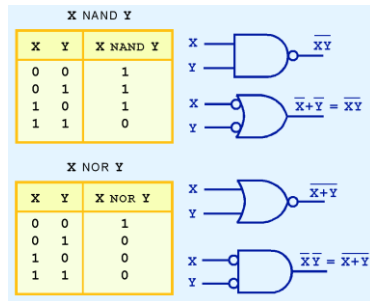- NAND and NOR are two very important gates.




22

22

Logic Gates

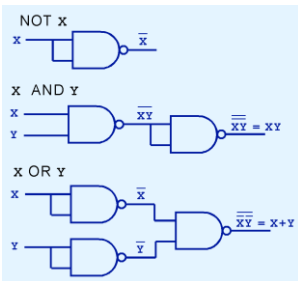- NAND and NOR are known as **universal gates** because they are inexpensive to manufacture, and any Boolean function can be constructed using only NAND or only NOR gates.



23

23

Logic Gates

- Gates can have multiple inputs and more than one output.
- A second output can be provided for the complement of the operation.



24

24

Digital Components

- The main thing to remember is that combinations of gates implement Boolean functions.
- The circuit below implements the Boolean function: $F(X, Y, Z) = X + \bar{Y}Z$



– We simplify our Boolean expressions so that we can create simpler circuits.

25

25

Combinational Circuits

- We have designed a circuit that implements the Boolean function:

$$F(X, Y, Z) = X + \bar{Y}Z$$

- This circuit is an example of a **combinational logic circuit**.
- Combinational logic circuits** produce a specified output (almost) at the instant when input values are applied.

26

26

Combinational Circuits

- Combinational logic circuits give us many useful devices.

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- One of the simplest is the **half adder**, which finds the sum of two bits.

- We can gain some insight as to the construction of a **half adder** by looking at its truth table


27

27

Combinational Circuits

- As we see, the sum can be found using the **XOR** operation and the carry using the **AND** operation.

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

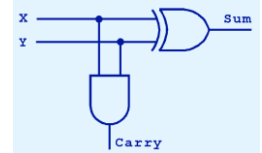


28

28

Combinational Circuits

- We can change our half adder into to a full adder by including gates for processing the carry bit.
- The truth table for a full adder and its implementation:

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

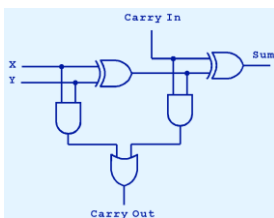


29

29

Combinational Circuits

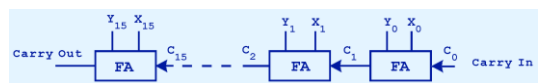- Just as we combined half adders to make a full adder, full adders can be connected in series.
- The carry bit **ripples** from one adder to the next; hence, this configuration is called a **ripple-carry adder**.



– Today's systems employ more efficient adders.

30

30

Combinational Circuits

- Decoders are another important type of combinational circuit.
 - Among other things, they are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.




- Address decoders with n inputs can select any of 2^n locations.

31

31

Combinational Circuits

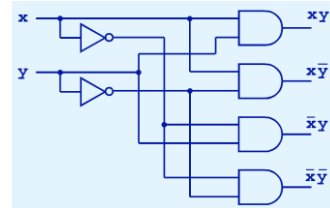- This is what a 2-to-4 decoder looks like on the inside.




- If $x = 0$ and $y = 1$, which output line is enabled?

32

32

Combinational Circuits

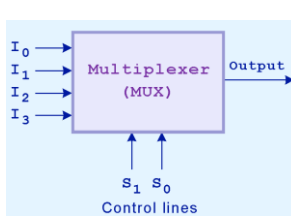- A multiplexer does just the opposite of a decoder.
- It selects a single output from several inputs.




- The particular input chosen for output is determined by the value of the multiplexer's control lines.
- To be able to select among n inputs, $\log_2 n$ control lines are needed.

33

33

Combinational Circuits

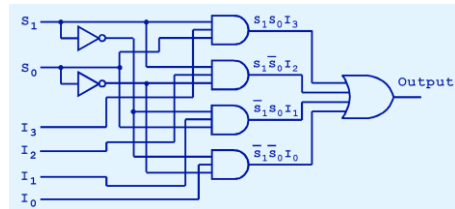- This is what a 4-to-1 multiplexer looks like on the inside.



- If $S_0 = 1$ and $S_1 = 0$, which input is transferred to the output?

34

34

Sequential Circuits

- Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.
- There are other times, however, when we need a circuit to change its value with consideration to its current state as well as its inputs.
 - These circuits have to remember their current state.
- Sequential logic circuits provide this functionality for us.

35

35

Sequential Circuits

- As the name implies, sequential logic circuits require a means by which events can be sequenced.
- State changes are controlled by clocks.
 - A clock is a special circuit that sends electrical pulses through a circuit.
- Clocks produce electrical waveforms such as the one shown below.




36

36

Sequential Circuits

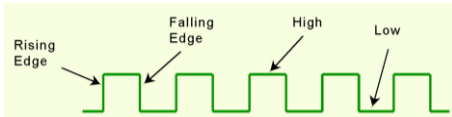- State changes occur in sequential circuits only when the clock ticks.
- Circuits can change state on the rising edge, falling edge, or when the clock pulse reaches its highest voltage.




37

37

Sequential Circuits

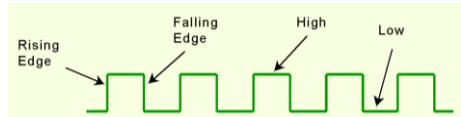- Circuits that change state on the rising edge, or falling edge of the clock pulse are called **edge-triggered**.
- **Level-triggered** circuits change state when the clock voltage reaches its highest or lowest level.




38

38

Sequential Circuits

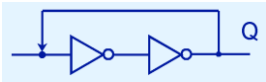- To retain their state values, sequential circuits rely on **feedback**.
- Feedback in digital circuits occurs when an output is looped back to the input.
- A simple example of this concept is shown below.




– If Q is 0 it will always be 0, if it is 1, it will always be 1. Why?

39

39

Sequential Circuits

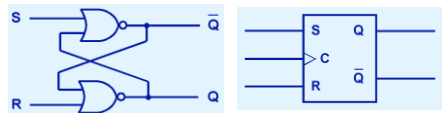- You can see how feedback works by examining the most basic sequential logic components, the SR flip-flop.
- The SR stands for **set/reset**.
- The internals of an SR flip-flop are shown below, along with its block diagram.




40

40

Sequential Circuits

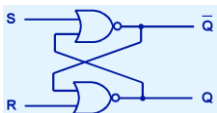- The behavior of an SR flip-flop is described by a characteristic table.



S	R	Q(t+1)
0	0	Q(t) (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined

- Q(t) means the value of the output at time t.
- Q(t+1) is the value of Q after the next clock pulse.

41

41

Sequential Circuits

- The SR flip-flop actually has three inputs:
- S, R, and its **current output, Q**.

Present State			Next State
S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	undefined
1	1	1	undefined


- Thus, we can construct a truth table for this circuit, as shown at the left.
- Notice the two undefined values.
- When both S and R are 1, the SR flip-flop is unstable.

42

42

Sequential Circuits

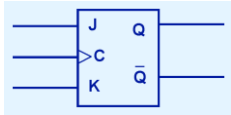- If we can be sure that the inputs to an SR flip-flop will never both be 1, we will never have an unstable circuit. This may not always be the case.
- The SR flip-flop can be modified to provide a stable state when both inputs are 1.



– This modified flip-flop is called a JK flip-flop, shown at the left.


- The JK is in honor of Jack Kilby.

43

43

Sequential Circuits

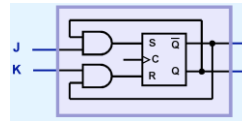- At the left, we see how an SR flip-flop can be modified to create a JK flip-flop.
- The characteristic table indicates that the flip-flop is stable for all inputs.




J	K	Q(t+1)
0	0	Q(t) (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	Q-bar(t)

44

44

Sequential Circuits

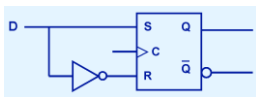- Another modification of the SR flip-flop is the D flip-flop, shown below with its characteristic table.
 - You will notice that the output of the flip-flop remains the same during subsequent clock pulses.
 - The output changes only when the value of D changes.




D	Q(t+1)
0	0
1	1

45

45

Sequential Circuits

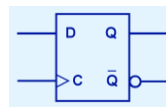- The D flip-flop is the fundamental circuit of computer memory.
 - D flip-flops are usually illustrated using the block diagram shown below.
- The next slide shows how these circuits are combined to create a register.




D	Q(t+1)
0	0
1	1

46

46

Sequential Circuits

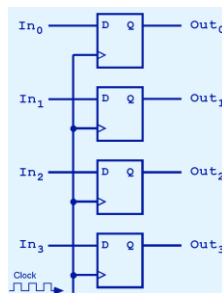- This illustration shows a 4-bit register consisting of D flip-flops.
- You will usually see its block diagram (below) instead.




47

47

Sequential Circuits

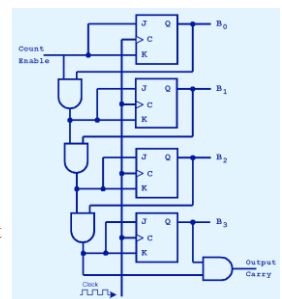- A binary counter is another example of a sequential circuit.
- The low-order bit is complemented at each clock pulse.
 - Whenever it changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops.



48

48

Designing Circuits

- We have seen digital circuits from two points of view:
 - **Digital analysis**
 - explores the relationship between a circuit's inputs and its outputs.
 - **Digital synthesis**
 - creates logic diagrams using the values specified in a truth table.
- Digital systems designers must also be mindful of the physical behaviors of circuits to include minute propagation delays that occur between the time when a circuit's inputs are energized and when the output is accurate and stable.

49

49

Designing Circuits

- Digital designers rely on specialized software to create efficient circuits.
 - Thus, software is an enabler for the construction of better hardware.
- Of course, software is in reality a collection of algorithms that could just as well be implemented in hardware.
 - Recall the Principle of Equivalence of Hardware and Software.

50

50

Designing Circuits

- When we need to implement a simple, specialized algorithm and its execution speed must be as fast as possible, a hardware solution is often preferred.
- This is the idea behind **embedded systems**, which are small special-purpose computers that we find in many everyday things.
- **Embedded systems** require special programming that demands an understanding of the operation of digital circuits, the basics of which you have learned in this chapter.

51

51

Conclusion

- Computers are implementations of **Boolean logic**.
- **Boolean functions** are completely described by **truth tables**.
- Logic gates are small circuits that implement Boolean operators.
- The basic gates are **AND**, **OR**, and **NOT**.
- The **XOR** gate is very useful in parity checkers and adders.
- The “**universal gates**” are **NOR**, and **NAND**.

52

52

Conclusion

- Computer circuits consist of **combinational logic circuits** and **sequential logic circuits**.
- Combinational circuits produce outputs (almost) immediately when their inputs change.
- Sequential circuits require clocks to control their changes of state.
- The basic sequential circuit unit is the flip-flop:
 - The behaviors of the **SR**, **JK**, and **D** flip-flops are the most important to know.

53

53