

## BLM1612 - Circuit Theory

Prof. Dr. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

[www.yildiz.edu.tr/~naydin](http://www.yildiz.edu.tr/~naydin)

Op-Amps

1

## Operational Amplifiers

(Op-Amps)

2

## Objectives of Lecture

- Describe how an ideal operational amplifier (op-amp) behaves.
- Define voltage gain, current gain, transresistance gain, and transconductance gain.
- Explain the operation of an ideal op amp in a voltage comparator and inverting amplifier circuit.
  - Show the effect of using a real op-amp.
- Apply the ‘almost ideal’ op-amp model in the following circuits:
  - Inverting Amplifier
  - Noninverting Amplifier
  - Voltage Follower
  - Summing Amplifier
  - Difference Amplifier
  - Cascaded Amplifiers

3

## The Operational Amplifier

- An **operational amplifier (Op-Amp)** is a DC-coupled **high-gain** electronic **voltage amplifier** with a **differential input** and, usually, a **single-ended output**.
- An Op-Amp produces an output potential (relative to circuit ground) that is typically hundreds of thousands of times larger than the potential difference between its input terminals.
- The operational amplifier finds daily usage in a large variety of electronic applications.




4

## Op Amps Applications

- Audio amplifiers
  - Speakers and microphone circuits in cell phones, computers, mpg players, boom boxes, etc.
- Instrumentation amplifiers
  - Biomedical systems including heart monitors and oxygen sensors.
- Power amplifiers
- Analog computers
  - Combination of integrators, differentiators, summing amplifiers, and multipliers


5

## Symbols for Ideal and Real Op Amps

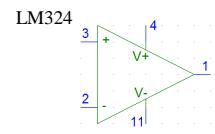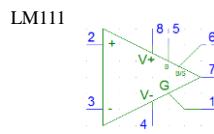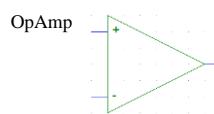


6


## Terminals on an Op Amp

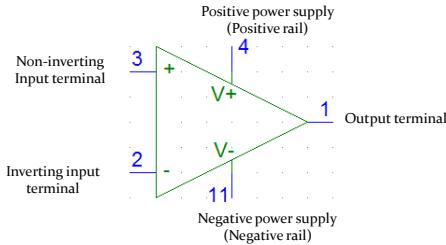

## Op Amp Equivalent Circuit

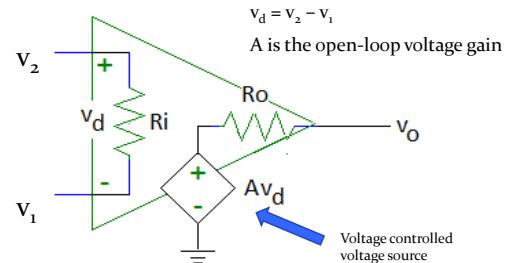

## The Operational Amplifier

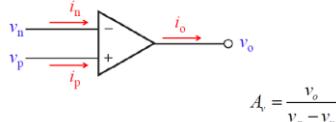

Function of the op amp:

to amplify the voltage difference  $v_p - v_n$  by  $A_v > 10^6$  with external feedback such that

$$v_n \approx v_p$$

$$i_n = i_p \approx 0$$

### Ideal Op-Amp Rules

- No current ever flows into either input terminal.
- There is no voltage difference between the two input terminals.

## Typical Op-Amp Parameters

Parameter	Variable	Typical Ranges	Ideal Values
Open-Loop Voltage Gain	A	$10^5$ to $10^8$	$\infty$
Input Resistance	$R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output Resistance	$R_o$	10 to 100 $\Omega$	0 $\Omega$
Supply Voltage	$V_{CC}/V^+$ $-V_{CC}/V^-$	5 to 30 V -30V to 0V	N/A N/A


9

10

## How to Find These Values

- Component Datasheets
  - Many manufacturers have made these freely available on the internet
  - Example: LM741, LM 324, etc.

## The Operational Amplifier

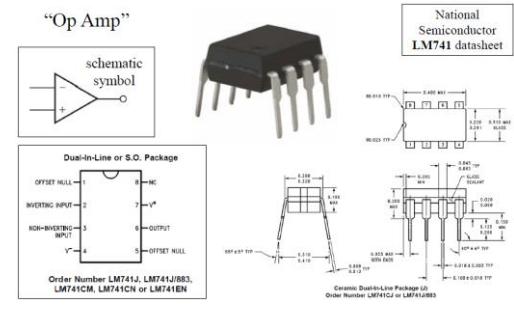

11

12

<http://www.national.com/ds/LM/LM124.pdf> - Windows Internet Explorer

National Semiconductor

LM124/LM224/LM324/LM2902  
Low Power Quad Operational Amplifiers

General Description

The LM124 series consists of four independent, high gain, internally frequency compensated operational amplifiers which are designed to operate from a single power supply over a wide range of voltages. Operation from split power supplies is also possible. The low power quad supply current is a fraction of the maximum of the individual power supply voltages.

Applications can include transducer amplifiers, DC gain blocks and all the conventional op amp circuits which can be more easily implemented in single power supply systems. The LM124 series is designed to be operated off of the standard +5V power supply voltage which is used in digital systems and will easily provide the required interface electronics without requiring the additional ±15V power supplies.

Unique Characteristics

- In the linear mode the input common-mode voltage range includes ground and the output voltage can also include frequencies compensated to unity gain
- Large DC voltage gain: 100 dB
- Wide bandwidth (unity gain): 1 MHz
- Very low current drain (700  $\mu$ A)—essentially independent of supply voltage
- Power drain suitable for battery operation

Features

- Four internally compensated op amps in a single package
- Allows direct sensing near GND and  $V_{OUT}$  also goes to GND
- Compatible with all forms of logic
- Power drain suitable for battery operation

LM124/LM224/LM324/LM2902 Low Power Quad

dB

- Decibels

$$\text{Since } P = V^2/R$$

$$10 \log (P/P_{ref}) \text{ or } 20 \log (V/V_{ref})$$

In this case:

$$20 \log (V_o/V_{in}) = 20 \log (A) = 100$$

$$A = 10^5 = 100,000$$

14

<http://www.national.com/ds/LM/LM124.pdf> - Windows Internet Explorer

Electrical Characteristics

$V^+ = +5.0V$ , (Note 7), unless otherwise stated

Parameter	Condition	LM124A	LM224A	LM324A							
		Min.	Typ.	Max.	Min.	Typ.	Max.	Min.	Typ.	Max.	Units
Input Offset Voltage	(Note 8) $T_A = 25^\circ C$	1	2	1	3	2	3	2	3	mV	
Input Bias Current	$I_{IN1} = I_{IN2} = V_{CM} = 0V$ , $T_A = 25^\circ C$	20	50	40	80	45	100	nA			
Input Offset Current	$I_{IN1} = I_{IN2} = V_{CM} = 0V$ , $T_A = 25^\circ C$	2	10	2	15	5	30	nA			
Input Common-Mode Voltage Range (Note 10)	$V^+ = 30V$ , ( $LM2902$ , $V^+ = 26V$ ), $T_A = 25^\circ C$	0	$V^- = 1.5$	0	$V^- = 1.5$	0	$V^- = 1.5$	V			
Supply Current	Over Full Temperature Range: $R_L = \infty$ On All Op Amps $V^+ = 30V$ ( $LM2902$ $V^+ = 26V$ ) $V^- = 0V$	1.5	3	1.5	3	1.5	3	mA			
Large Signal Voltage Gain	$V^+ = 15V$ , $R_L = 2k\Omega$ $V^- = 1V$ to $11V$ , $T_A = 25^\circ C$	50	100	50	100	25	100	V/mV			
Common-Mode Rejection Ratio	$ DC, V_{CM} = 0V$ to $V^- = 1.5V$	70	85	70	85	65	95				

3 www.national.com

## Large Signal Voltage Gain = A

- Typical


$$- A = 100 \text{ V/mV} = 100\text{V}/0.001\text{V} = 100,000$$

- Minimum

$$- A = 25 \text{ V/mV} = 25 \text{ V}/0.001\text{V} = 25,000$$

16

## Caution – A is Frequency Dependent

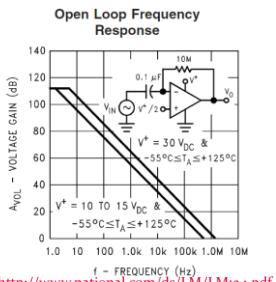


17

## Modifying Gain in Pspice OpAmp

- Place part in a circuit
- Double click on component
- Enter a new value for the part attribute called GAIN

18

## OrCAD Schematics

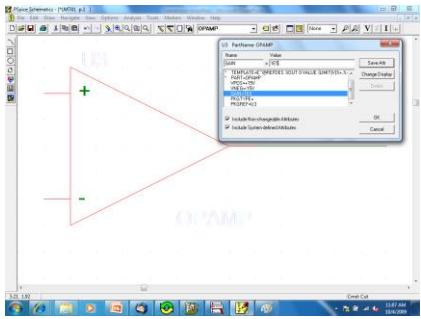

## Open Circuit Output Voltage


- Open Circuit Output Voltage

$$v_o = A v_d$$

- Ideal Op-Amp

$$v_o = \infty (v_d)$$

- Saturation in real Op-Amp

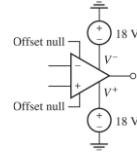

– An op-amp requires power supplies.

– Usually, equal and opposite voltages are connected to the  $V^+$  and  $V^-$  terminals.

– Typical values are 5 to 24 volts.

– The power supply ground must be the same as the signal ground.

- Above,  $+18V$  is connected to  $V^+$  and  $-18V$  is connected to  $V^-$

20


## Open Circuit Output Voltage

- Real Op Amp

	Voltage Range	Output Voltage
Positive Saturation	$A v_d > V^+$	$v_o \sim V^+$
Linear Region	$V^- < A v_d < V^+$	$v_o = A v_d$
Negative Saturation	$A v_d < V^-$	$v_o \sim V^-$

The voltage produced by the dependent voltage source inside the op amp is limited by the voltage applied to the positive and negative rails.


## Voltage Transfer Characteristic

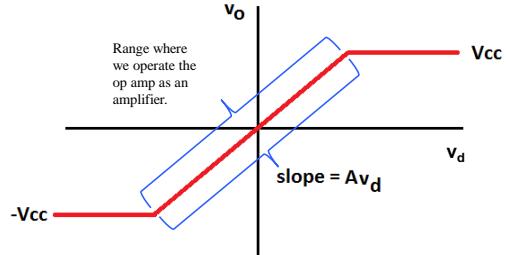

22
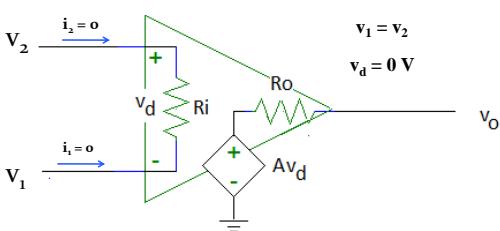
## Ideal Op-Amp

Because  $R_i$  is equal to  $\infty \Omega$ , the voltage across  $R_i$  is  $0V$ .



23

## Almost Ideal Op Amp

- $R_i = \infty \Omega$

– Therefore,  $i_1 = i_2 = 0A$

- $R_o = 0 \Omega$

- Usually,  $v_d = 0V$  so  $v_1 = v_2$


– The op-amp forces the voltage at the inverting input terminal to be equal to the voltage at the noninverting input terminal if there is some component connecting the output terminal to the inverting input terminal.

- Rarely is the op-amp limited to  $V^- < v_o < V^+$ .

– The output voltage is allowed to be as positive or as negative as needed to force  $v_d = 0V$ .

24

## Example 01: Voltage Comparator...

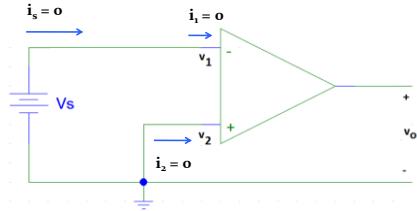

Note that the inverting input and non-inverting input terminals have rotated in this schematic.

25


## ...Example 01...

- The internal circuitry in the op-amp tries to force the voltage at the inverting input to be equal to the non-inverting input.

As we will see shortly, a number of op-amp circuits have a resistor between the output terminal and the inverting input terminals to allow the output voltage to influence the value of the voltage at the inverting input terminal.

26

## ...Example 01: Voltage Comparator

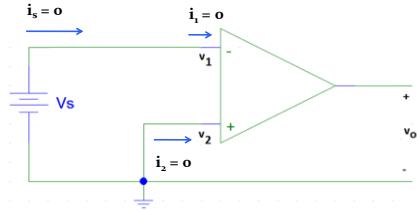


When Vs is equal to 0V, Vo = 0V.  
When Vs is smaller than 0V, Vo = V+.  
When Vs is larger than 0V, Vo = V-.

27

## Electronic Response


- Given how an op-amp functions, what do you expect Vo to be if v2 = 5V when:

1. Vs = 0V?
2. Vs = 5V?
3. Vs = 6V?

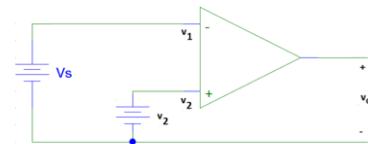


28

## Example 02: Closed Loop Gain...

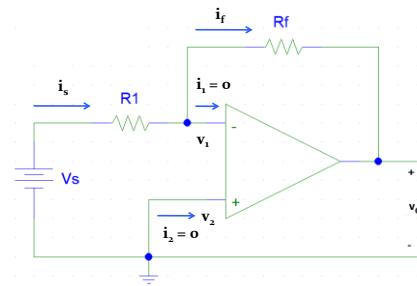

29


## ...Example 02...

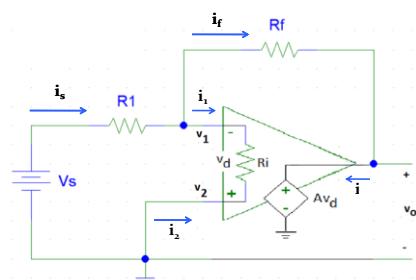

For an almost ideal op amp,  $R_i = \infty \Omega$  and  $R_o = 0 \Omega$ . The output voltage will never reach  $V^+$  or  $V^-$ .


30

## ...Example 02...

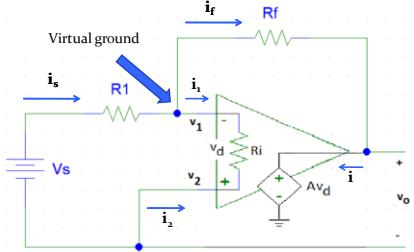


The op amp outputs a voltage  $v_o$  such that  $v_1 = v_2$ .

## ...Example 02...

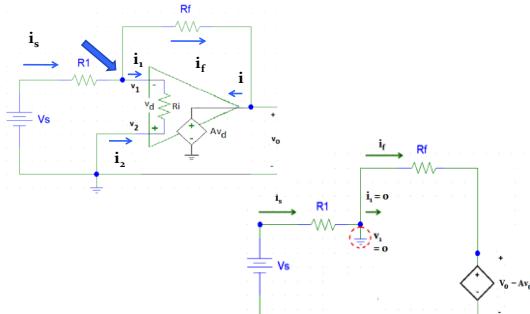


32

## ...Example 02: Closed Loop Gain

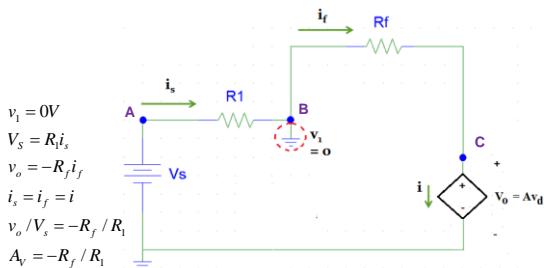

This circuit is known as an inverting amplifier.

## Types of Gain

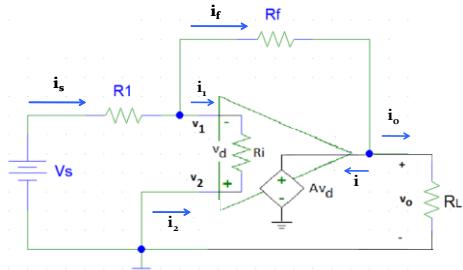


34

## Types of Closed Loop Gain

Gain	Variable Name	Equation	Units
Voltage Gain	$A_V$	$v_o/v_s$	None or V/V
Current Gain	$A_I$	$i_o/i_s$	None or A/A
Transresistance Gain	$A_R$	$v_o/i_s$	V/A or $\Omega$
Transconductance Gain	$A_G$	$i_o/v_s$	A/V or $\Omega^{-1}$
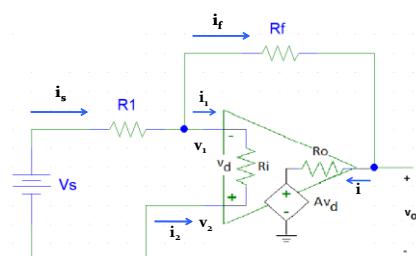
## Example 03: Closed Loop Gain with Real Op-Amp...



35

### ...Example 03

$$\begin{aligned} i_s &= i_1 + i_f \\ i &= i_f \\ -i_1 &= i_2 \end{aligned}$$

$$v_d = v_2 - v_1 = R_i (-i_1) = R_i (i_2)$$

$$V_o = A v_d - R_o (-i)$$

$$V_s = R_i (i_s) - v_d$$

$$V_s = R_i (i_s) + R_f (i_f) + V_o$$

$$V_o / V_s = (-R_f / R_i) \{ A b / [1 + A b] \}, \text{ where } b = R_i / (R_i + R_f)$$

37

### Summary


- The output of an ideal op-amp is a voltage from a dependent voltage source that attempts to force the voltage at the inverting input terminal to equal the voltage at the non-inverting input terminal.
  - Almost ideal op-amp:** Output voltage limited to the range between  $V^+$  and  $V^-$ .
- Ideal op amp is assumed to have  $R_i = \infty \Omega$  and  $R_o = 0 \Omega$ .
  - Almost ideal op-amp:**  $v_d = 0 \text{ V}$  and the current flowing into the output terminal of the op-amp is as much as required to force  $v_1 = v_2$  when  $V^+ < v_o < V^-$ .
- Operation of an op-amp was used in the analysis of voltage comparator and inverting amplifier circuits.
  - Effect of  $R_i < \infty \Omega$  and  $R_o > 0 \Omega$ :** Was shown.

38

### Op-Amp Circuits

39


### Almost Ideal Op-Amp Model

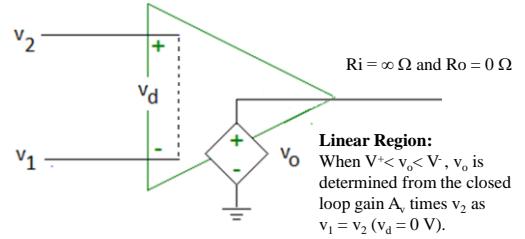

**Saturation:**  
When  $A_v v_2 \geq V^+$ ,  $v_o = V^+$ .  
When  $A_v v_2 \leq V^-$ ,  $v_o = V^-$ .


40

### Example 04: Inverting Amplifier...

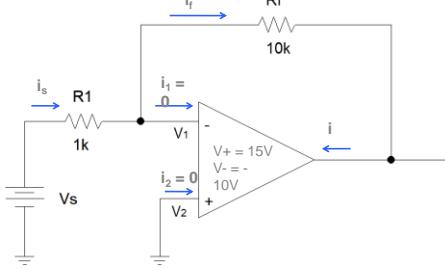

41

### ...Example 04...

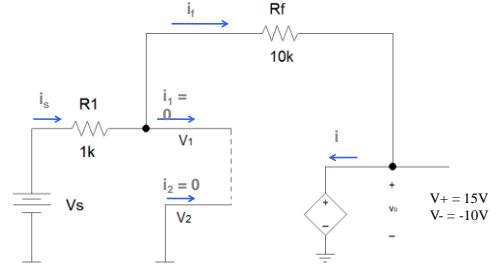


42

### ...Example 04...

- Closed loop gains are dependent on the values of  $R_1$  and  $R_f$ .
  - Therefore, you have to calculate the closed loop gain for each new problem.

### ...Example 04...

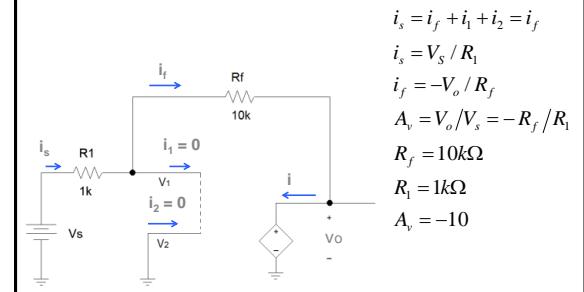


44

### ...Example 04...

- Since  $A_v = -10$ 
  - If  $V_s = 0V$ ,  $V_o = -10(0V) = 0V$
  - If  $V_s = 0.5V$ ,  $V_o = -10(0.5V) = -5V$
  - If  $V_s = 1V$ ,  $V_o = -10(1V) = -10V$
  - If  $V_s = 1.1V$ ,  $V_o = -10(1.1V) < V^-$ ,  $V_o = -10V$
  - If  $V_s = -1.2V$ ,  $V_o = -10(-1.2V) = +12V$
  - If  $V_s = -1.51V$ ,  $V_o = -10(-1.51V) > V^+$ ,  $V_o = +15V$


### ...Example 04

- Voltage transfer characteristic

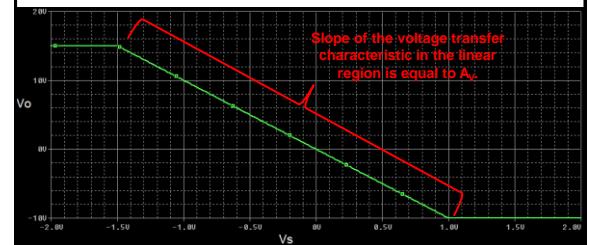


46
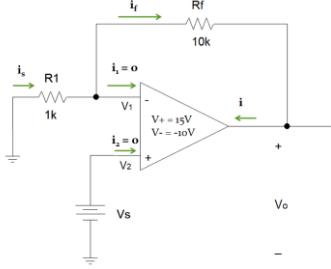
### Example 05: Noninverting Amplifier...




47

### ...Example 05...

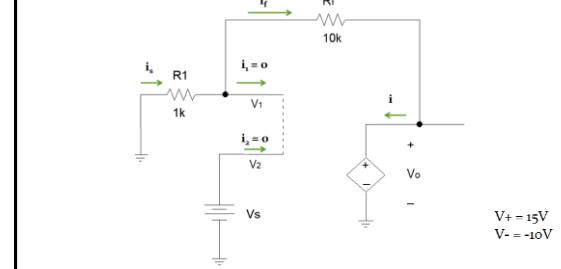


48

### ...Example 05...

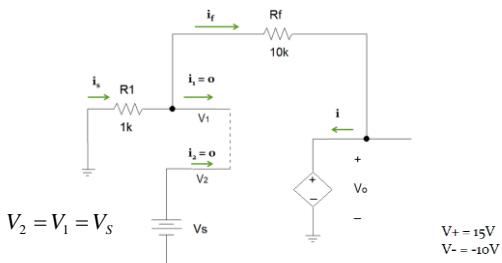


49

### ...Example 05...

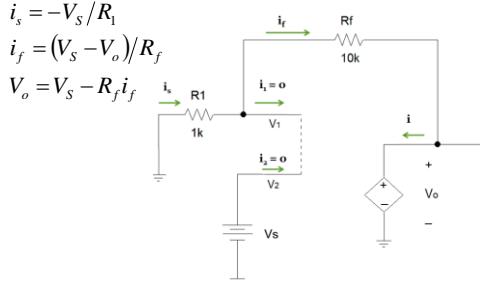


50
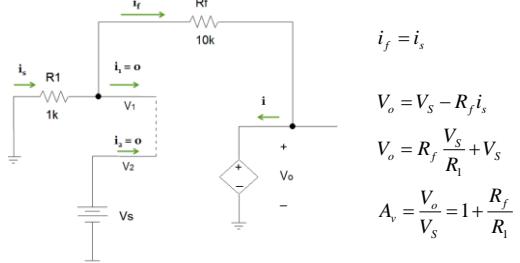
### ...Example 05: Noninverting Amplifier...



51


### ...Example 05...

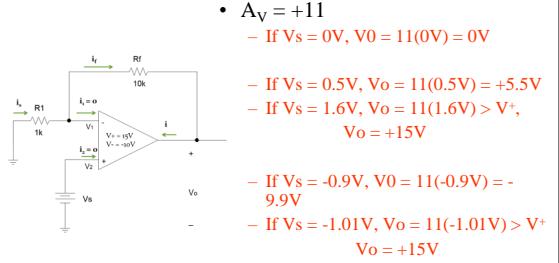

52

### ...Example 05

- Voltage transfer characteristic

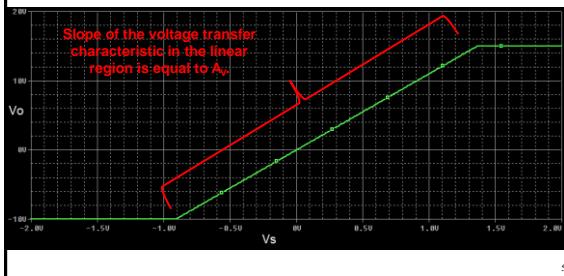


53

### Example 06: Voltage Follower


A voltage follower is a noninverting amplifier where  $R_f = 0\Omega$  and  $R_l = \infty\Omega$ .

$$V_o/V_s = 1 + R_f/R_l = 1 + 0 = 1$$

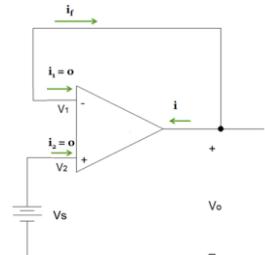

54


### Example 07: Summing Amplifier...

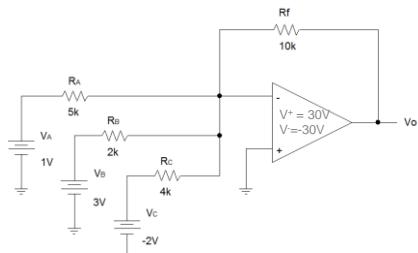

A summing amplifier is an inverting amplifier with multiple inputs.

55


### ...Example 07...

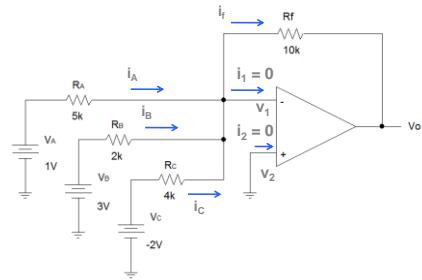

We apply superposition to obtain a relationship between  $V_o$  and the input voltages.


56

### ...Example 07...

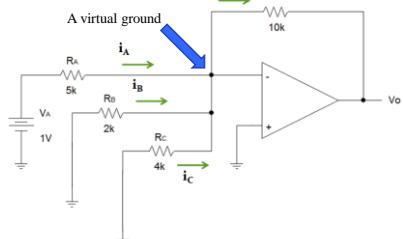


57

### ...Example 07...

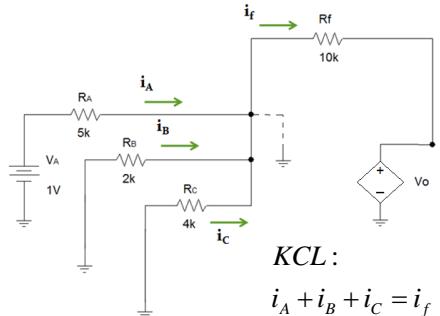

58

### ...Example 07...

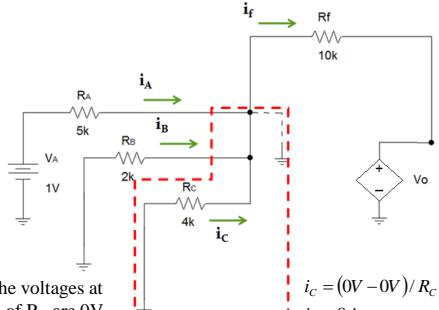


Note that the voltages at both nodes of  $R_C$  are 0V.  
 $i_c = (0V - 0V)/R_c$   
 $i_c = 0A$

59

### ...Example 07...


60

### ...Example 07...

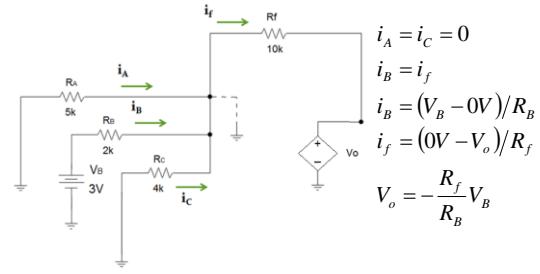


61

### ...Example 07...

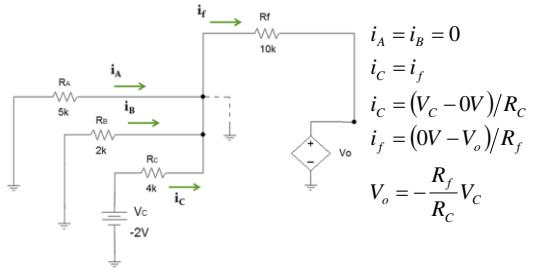


62

### ...Example 07

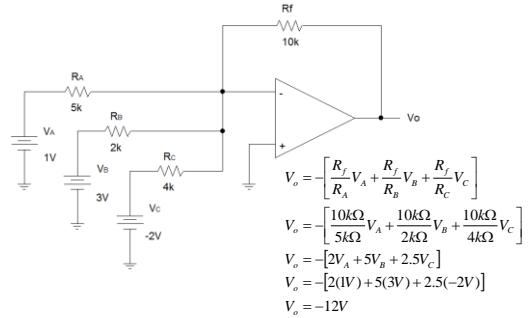


63

### Example 08: Difference Amplifier...

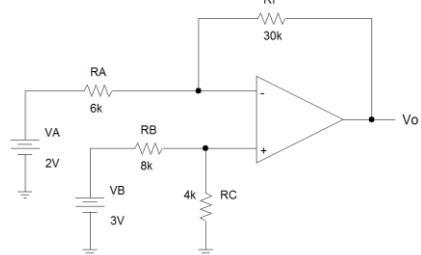


64

### ...Example 08...

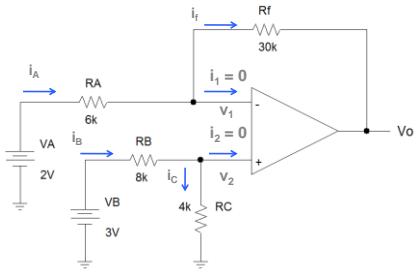


65

### ...Example 08...

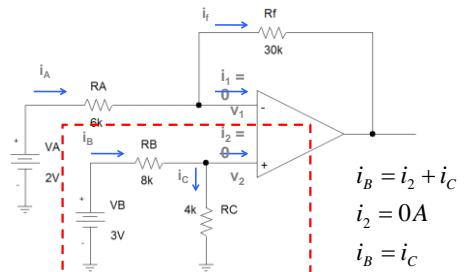

66

### ...Example 08...

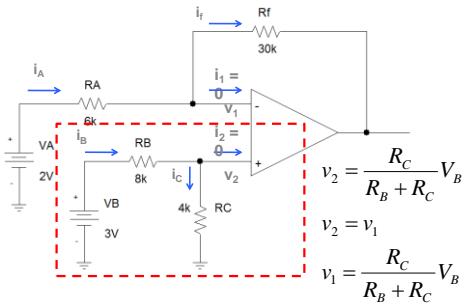

67

### ...Example 08...

$V_1 = \frac{R_C}{R_B + R_C} V_B$

$i_A = \frac{V_A - V_1}{R_A}$

$i_f = \frac{V_1 - V_o}{R_F}$

$V_o = V_B - V_1$

68

### ...Example 08...

$V_o = \frac{R_f}{R_A} \left( \frac{1 + R_A/R_f}{1 + R_B/R_C} \right) V_B - \frac{R_f}{R_A} V_A$

$V_o = \frac{30k\Omega}{6k\Omega} \left( \frac{1 + 6k\Omega/30k\Omega}{1 + 8k\Omega/4k\Omega} \right) (3V) - \frac{30k\Omega}{6k\Omega} (2V)$

$V_o = -4V$


69

### ...Example 08

- If  $R_A/R_f = R_B/R_C$
- $V_o = \frac{R_f}{R_A} (V_B - V_A)$
- And if  $R_A = R_f$
- $V_o = V_B - V_A$

70


### Example 09: Cascading Op Amps...

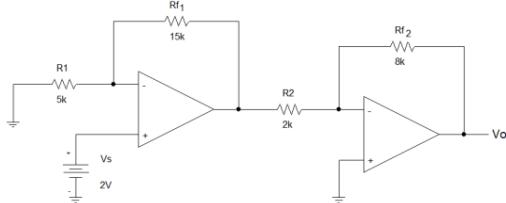

71
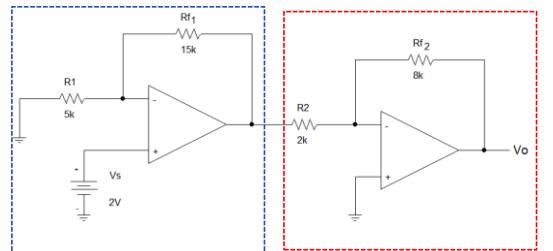
### ...Example 09...


- Treat as two separate amplifier circuits




72

## ...Example 09...

1st Circuit

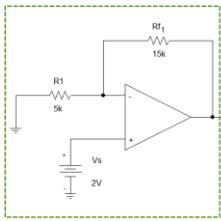


2nd Circuit

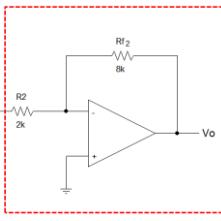

73

## ...Example 09...

- It is a noninverting amplifier.

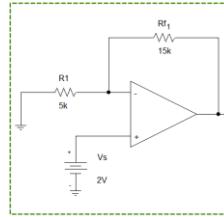


$$V_{o1} = \left(1 + \frac{R_{f1}}{R_1}\right) V_s$$

$$A_{V1} = \frac{V_{o1}}{V_s} = \left(1 + \frac{R_{f1}}{R_1}\right)$$

74

## ...Example 09...

- It is an inverting amplifier.

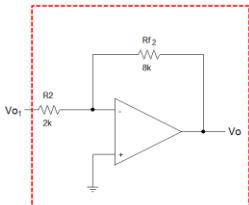


$$V_o = -\frac{R_{f2}}{R_2} V_{o1}$$

$$A_{V2} = \frac{V_o}{V_{o1}} = -\frac{R_{f2}}{R_2}$$

75
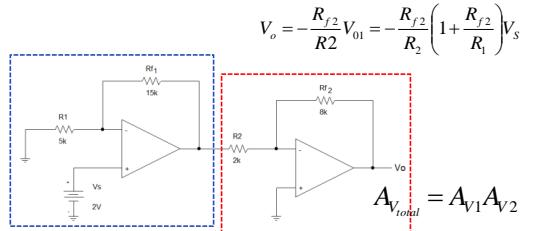
## ...Example 09...

- The gain of the cascaded amplifiers is the multiplication of the two individual amplifiers



$$A_{V_{total}} = A_{V1} A_{V2}$$


76

## Instrumentation amplifier

- This device allows precise amplification of small voltage differences:

$$V_{out} = K(v_+ - v_-)$$

$$R_4/R_3 = R_2/R_1 = K.$$

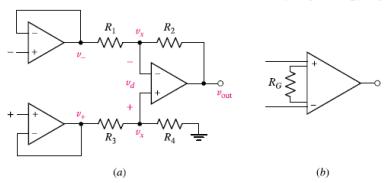

(a) The basic instrumentation amplifier. (b) Commonly used symbol.

77

## Summary

- The ‘almost ideal’ op amp model:

- $R_i = \infty \Omega$ .
  - $i_1 = i_2 = 0A; v_1 = v_2$
  - $R_o = 0 \Omega$ .
    - No power/voltage loss between the dependent voltage source and  $v_o$ .
  - The output voltage is limited by the voltages applied to the positive and negative rails.
    - $V^+ \geq v_o \geq V^-$


- This model can be used to determine the closed loop voltage gain for any op amp circuit.

- Superposition can be used to solve for the output of a summing amplifier.


- Cascaded op amp circuits can be separated into individual amplifiers and the overall gain is the multiplication of the gain of each amplifier.

78

## Summary of Basic Op Amp Circuits

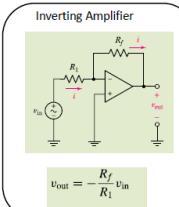


$$v_{out} = -\frac{R_f}{R_1} v_{in}$$

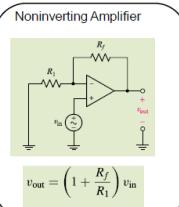

$$v_{out} = \left(1 + \frac{R_f}{R_1}\right) v_{in}$$

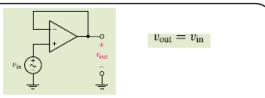
Voltage Follower (also known as a Unity Gain Amplifier)



$$v_{out} = v_{in}$$


## Summary of Basic Op Amp Circuits

Summing Amplifier

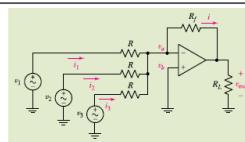

$$v_{out} = -\frac{R_f}{R} (v_1 + v_2 + v_3)$$

Difference Amplifier

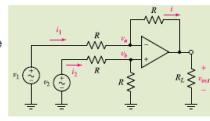

$$v_{out} = v_2 - v_1$$

79

80