


BLM1612 - Circuit Theory

Examples

1

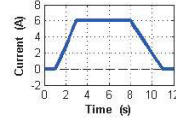Example 01

- Given the following current graph through an element, what is the net charge that passes through the element between $t = 4$ and $t = 8$ seconds?



$$q = \int_{t_1}^{t_2} i dt = \int_4^8 6 dt = 6t \Big|_4^8 = 6(8 - 4) = 24 \text{ C}$$


– or for constant current

$$q = i \times \Delta t = 6(8 - 4) = 24 \text{ C}$$

2

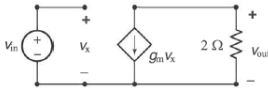Example 02

- In the circuit below, $v_{in} = 3\sin(\omega t)$ mV and $g_m = 10$ A/V. Determine v_{out} .



$$v_{out} = -g_m v_x \times R$$


$$v_{out} = -10 \times 3\sin(\omega t) \times 2$$

$$v_{out} = -60\sin(\omega t) \text{ mV}$$

3

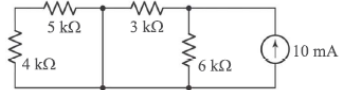Example 03

- In the circuit below, determine the power absorbed by the 5 kΩ resistor.



- Short circuit across 4 kΩ and 5 kΩ resistors.


– No current through 5 kΩ resistor.

- Therefore


$$P_{abs} = 0 \text{ W}$$

4

Example 04...

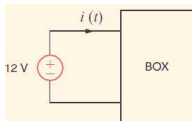

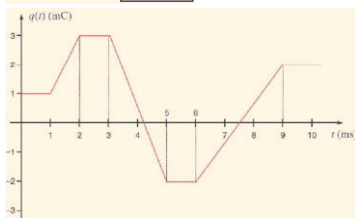- The charge that enters the BOX is given below. Calculate and sketch the current flowing into and the power absorbed by the BOX between 0 and 10 ms.



$$i(t) = \frac{dq(t)}{dt}$$

5

...Example 04...

Recall that current is related to charge by $i(t) = \frac{dq(t)}{dt}$. The current is equal to the slope of the charge waveform.

$$i(t) = 0 \quad 0 \leq t \leq 1 \text{ ms}$$

$$i(t) = \frac{3 \times 10^{-3} - 1 \times 10^{-3}}{2 \times 10^{-3} - 1 \times 10^{-3}} = 2 \text{ A} \quad 1 \leq t \leq 2 \text{ ms}$$

$$i(t) = 0 \quad 2 \leq t \leq 3 \text{ ms}$$

$$i(t) = \frac{-2 \times 10^{-3} - 3 \times 10^{-3}}{5 \times 10^{-3} - 3 \times 10^{-3}} = -2.5 \text{ A} \quad 3 \leq t \leq 5 \text{ ms}$$


$$i(t) = 0 \quad 5 \leq t \leq 6 \text{ ms}$$

$$i(t) = \frac{2 \times 10^{-3} - (-2 \times 10^{-3})}{9 \times 10^{-3} - 6 \times 10^{-3}} = 1.33 \text{ A} \quad 6 \leq t \leq 9 \text{ ms}$$

$$i(t) = 0 \quad t \geq 9 \text{ ms}$$

6

...Example 04...

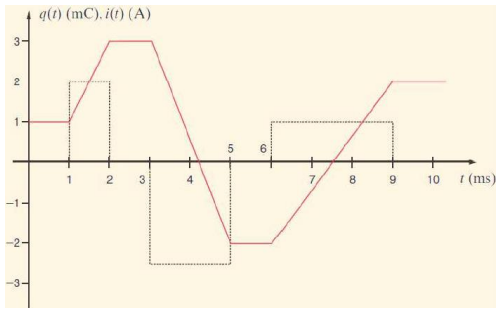


7

...Example 04


The power absorbed by the BOX is $12 \cdot i(t)$.

$$\begin{aligned}
 p(t) &= 12^0 = 0 & 0 \leq t \leq 1 \text{ ms} \\
 p(t) &= 12^1 = 24 \text{ W} & 1 \leq t \leq 2 \text{ ms} \\
 p(t) &= 12^0 = 0 & 2 \leq t \leq 3 \text{ ms} \\
 p(t) &= 12^2(-2.5) = -30 \text{ W} & 3 \leq t \leq 5 \text{ ms} \\
 p(t) &= 12^0 = 0 & 5 \leq t \leq 6 \text{ ms} \\
 p(t) &= 12^1 1.33 = 16 \text{ W} & 6 \leq t \leq 9 \text{ ms} \\
 p(t) &= 12^0 = 0 & t \geq 9 \text{ ms}
 \end{aligned}$$

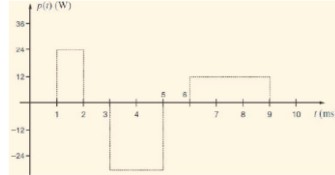

8

Example 05

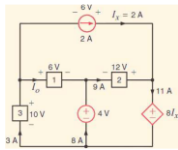

• Use Tellegen's theorem to find the current I_o in the network below.

$$\begin{aligned}
 P_{2A} &= (6)(-2) = -12 \text{ W} \\
 P_1 &= (6)(I_o) = 6I_o \text{ W} \\
 P_2 &= (12)(-9) = -108 \text{ W} \\
 P_3 &= (10)(-3) = -30 \text{ W} \\
 P_{4V} &= (4)(-8) = -32 \text{ W} \\
 P_{DS} &= (8I_o)(11) = (16)(11) = 176 \text{ W}
 \end{aligned}$$

Applying Tellegen's theorem yields

$$-12 + 6I_o - 108 - 30 - 32 + 176 = 0$$

or

$$6I_o + 176 = 12 + 108 + 30 + 32$$

Hence,

$$I_o = 1 \text{ A}$$

9

10