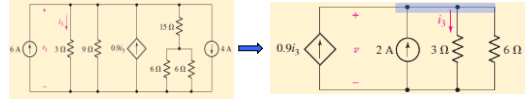


Examples

1

Example 06

- Calculate the power and voltage of the dependent source in the following Figure.



$$-0.9i_3 - 2 + i_3 + \frac{v}{6} = 0$$

$$v = 3i_3$$

$$i_3 = \frac{10}{3} \text{ A}$$


$$-v \times 0.9i_3 = -10(0.9)\left(\frac{10}{3}\right) = -30 \text{ W}$$

- Actually 30 W is supplied

2

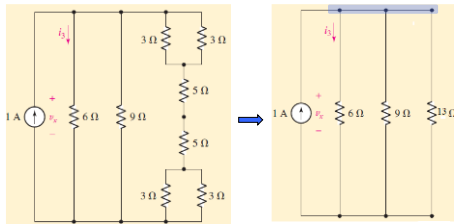Example 07

- For the circuit below, calculate the voltage v_x .




KCL yields $1 = v_x/6 + v_x/9 + v_x/13$
Solving, $v_x = 2.819 \text{ V}$

3

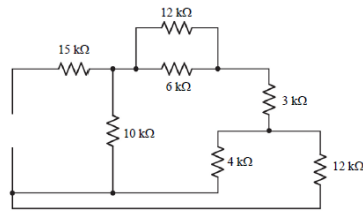Example 08

- Determine the equivalent resistance of this network between the open-circuit terminals.




- 20 kΩ

4

Example 09

- Determine i_3 for this circuit.

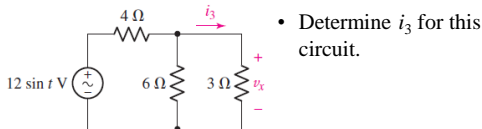

The total current flowing into the 3Ω-6Ω combination is

$$i(t) = \frac{12 \sin t}{4 + 3 \parallel 6} = \frac{12 \sin t}{4 + 2} = 2 \sin t \text{ A}$$

and thus the desired current is given by current division:


$$i_3(t) = (2 \sin t) \left(\frac{6}{6 + 3} \right) = \frac{4}{3} \sin t \text{ A}$$

5

Example 10


- $R_{AB} = ?$

- $R_{AB} = 5 \text{ k}\Omega$

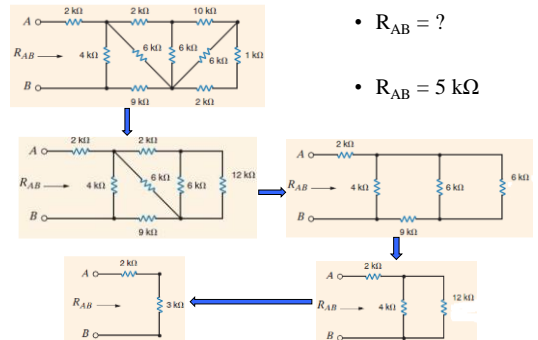


6

Example 11

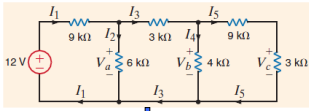

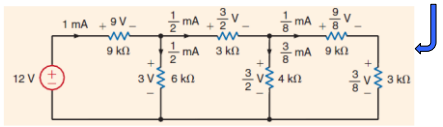- Find all the currents and voltages labeled in the ladder network.



7

8