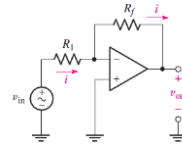


Examples

1

Example 27



- Determine v_{out} if $v_{in} = 2\text{ V}$, $R_f = 10\text{ k}\Omega$, and $R_1 = 2\text{ k}\Omega$.


$$v_n = v_p \quad i_n = i_p = 0$$

$$\text{KCL @ } v_n: \frac{v_{out} - v_n}{10} + \frac{2 - v_n}{2} - i_n = 0$$

$$v_p = 0$$


$$v_{out} = -10\text{ V}$$

(inverting amplifier)

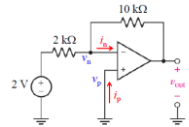


2

Example 28

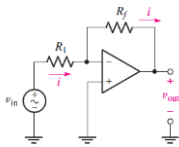


- Plot v_{out} if $v_{in} = 5 \sin 3t\text{ mV}$, $R_f = 47\text{ k}\Omega$, and $R_1 = 4.7\text{ k}\Omega$.

$$v_{out} = -\frac{R_f}{R_1} v_{in}$$

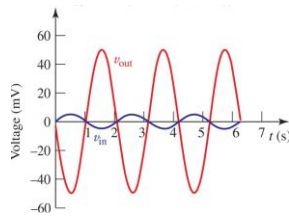

3


Example 29

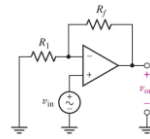

- Plot v_{out} if $v_{in} = 5 \sin 3t\text{ mV}$, $R_f = 47\text{ k}\Omega$, and $R_1 = 4.7\text{ k}\Omega$.

$$v_{out} = \left(\frac{R_f}{R_1} + 1\right) v_{in}$$

non-inverting amplifier

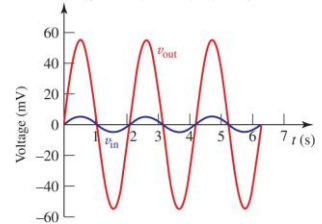

4

Example 30...

- Design a circuit to achieve: $v_{out} = 2v_1 - 3v_2 + 4v_3 - 6v_4$

$$v_{out} = \left(\frac{R_f}{R_x} + 1\right) v_{in}$$

non-inverting amp

$$v_{out} = \left(\frac{R_f}{R_x} + 1\right) v_{in}$$

non-inverting amp

$$v_{out} = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots\right)$$

inverting sum

$$v_{out} = v_2 - v_1$$

difference

$$v_{out} = -\left\{ \frac{R_f}{R_1} \left(-\frac{R_a}{R_a} v_1\right) + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} \left(-\frac{R_d}{R_c} v_3\right) + \frac{R_f}{R_4} v_4 \right\}$$

invert
invert

inverting sum

$$v_{out} = \frac{R_f R_b}{R_a R_n} v_1 - \frac{R_f}{R_2} v_2 + \frac{R_f R_d}{R_3 R_c} v_3 - \frac{R_f}{R_4} v_4$$

5

...Example 30...

$$v_{out} = \frac{R_f R_b}{R_1 R_n} v_1 - \frac{R_f}{R_2} v_2 + \frac{R_f R_d}{R_3 R_c} v_3 - \frac{R_f}{R_4} v_4$$

Choose $R_a = R_b = R_c = R_d = 2\text{ k}\Omega \dots$


$$v_{out} = \frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 - \frac{R_f}{R_4} v_4$$

Choose $R_f = 12\text{ k}\Omega \rightarrow R_1 = 6\text{ k}\Omega, R_2 = 4\text{ k}\Omega, R_3 = 3\text{ k}\Omega, R_4 = 2\text{ k}\Omega \dots$

$$v_{out} = \frac{12}{6} v_1 - \frac{12}{4} v_2 + \frac{12}{3} v_3 - \frac{12}{2} v_4$$

6


...Example 30

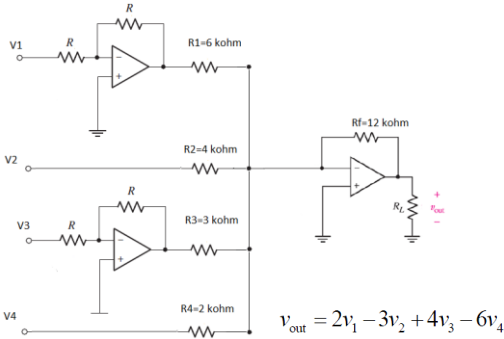

7

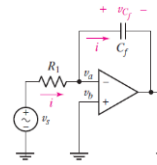Example 31

- An integrator circuit: Performing nodal analysis at the inverting input,



$$0 = \frac{v_u - v_i}{R_1} + i$$

We can relate the current i to the voltage across the capacitor,

$$i = C_f \frac{dv_{C_f}}{dt}$$

resulting in

$$0 = \frac{v_u - v_i}{R_1} + C_f \frac{dv_{C_f}}{dt}$$

Invoking ideal op amp rule 2, we know that $v_u = v_p = 0$, so

$$0 = \frac{-v_i}{R_1} + C_f \frac{dv_{C_f}}{dt}$$

Integrating and solving for v_{out} we obtain


$$v_{C_f} = v_i - v_{out} = 0 - v_{out} = -\frac{1}{R_1 C_f} \int_0^t v_i dt' + v_{C_f}(0)$$

$$v_{out} = -\frac{1}{R_1 C_f} \int_0^t v_i dt' - v_{C_f}(0)$$

8

Example 32

- An differentiator circuit

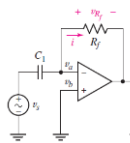

We begin by writing a nodal equation at the inverting input pin, with $v_{C_1} \triangleq v_u - v_i$:

$$0 = C_1 \frac{dv_{C_1}}{dt} + \frac{v_u - v_{out}}{R_f}$$

Invoking ideal op amp rule 2, $v_u = v_p = 0$. Thus,

$$C_1 \frac{dv_{C_1}}{dt} = \frac{v_{out}}{R_f}$$

Solving for v_{out} ,

$$v_{out} = R_f C_1 \frac{dv_{C_1}}{dt}$$


Since $v_{C_1} = v_u - v_i = -v_i$,

$$v_{out} = -R_f C_1 \frac{dv_i}{dt}$$

9

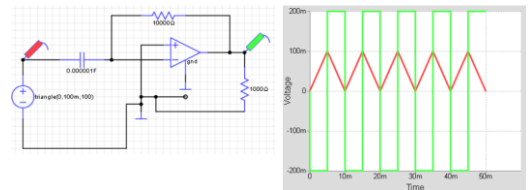Example 33


- A real Implementation:
 $C = 1 \mu\text{F}$, $R = 10 \text{ K}\Omega$, $RC = 0.01 \text{ (sec)}$
 $dv/dt = 100 \text{ mV/5 msec} = 20 \text{ V/sec}$



10

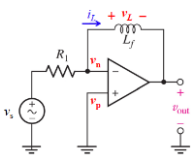Example 34

- Derive an expression for v_{out} in terms of v_s for the circuit.



$$v_u = v_p = 0, \quad i_u = i_p = 0$$

$$\frac{v_u - v_u}{R_1} - i_L = 0$$

$$\frac{v_u - v_u}{R_1} - \frac{1}{L_f} \int_{t_0}^t v_L \cdot dt' + i_u(t_0) = 0$$

$$\frac{v_u - v_u}{R_1} - \frac{1}{L_f} \int_{t_0}^t (v_u - v_{out}) \cdot dt' + i_u(t_0) = 0$$

$$\int_{t_0}^t v_{out} \cdot dt' + L_f \cdot i_u(t_0) = -\frac{L_f}{R_1} v_s$$

$$v_{out} = \frac{d}{dt} \left(-\frac{L_f}{R_1} v_s \right) =$$

11