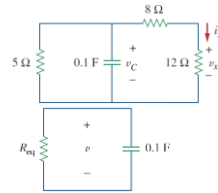


# BLM1612 - Circuit Theory

## Examples

1

### Example 35



- In the circuit, if  $v_C(0) = 15$  V, find  $v_C$ ,  $v_x$ ,  $i_x$  for  $t > 0$ .

$$R_{eq} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\tau = R_{eq}C = 4(0.1) = 0.4 \text{ s}$$

$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}$$


$$v_C = v = 15e^{-2.5t} \text{ V}$$

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$

2

### Example 36

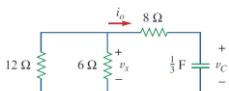


- In the circuit, if  $v_C(0) = 60$  V, find  $v_C$ ,  $v_x$ ,  $i_0$  for  $t \geq 0$ .

- Answer:  $60e^{-0.25t}$  V,  $20e^{-0.25t}$  V,  $-5e^{-0.25t}$  A.

3


### Example 37...

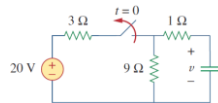

- The switch in the circuit has been closed for a long time, and it is opened at  $t = 0$ .

- Find  $v(t)$  for  $t \geq 0$ .
- Calculate the initial energy stored in the capacitor.

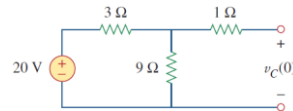- For  $t < 0$  the switch is closed; the capacitor is an open circuit to dc.




$$v_C(t) = \frac{9}{9 + 3}(20) = 15 \text{ V}$$

$$v_C(0) = V_0 = 15 \text{ V}$$

4
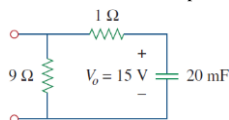
### ...Example 37

- For  $t > 0$  the switch is open; the voltage source is disconnected.



$$R_{eq} = 1 + 9 = 10 \Omega$$

$$\tau = R_{eq}C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

- The voltage across the capacitor for is


$$v(t) = v_C(0)e^{-t/\tau} = 15e^{-t/0.2} \text{ V} \quad \longrightarrow \quad v(t) = 15e^{-5t} \text{ V}$$

- The initial energy stored in the capacitor is

$$w_C(0) = \frac{1}{2}Cv_C^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2 = 2.25 \text{ J}$$

5

### Example 38

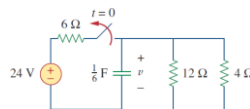


- If the switch in the circuit opens at  $t = 0$ , find  $v(t)$  for  $t \geq 0$  and  $w_C(0)$ .

- Answer:  $8e^{-2t}$  V, 5.333 J.


6

### Example 39...

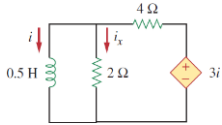

- In the circuit, if  $i(0) = 10$  A,  
- find  $i(t)$  and  $v_x, i_x(t)$  for  $t > 0$ .

- Method 1:

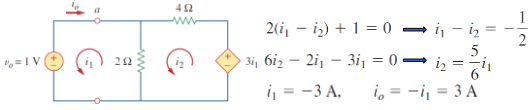

$$2(i_1 - i_2) + 1 = 0 \Rightarrow i_1 - i_2 = -\frac{1}{2}$$

$$6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$


$$i_1 = -3 \text{ A}, \quad i_o = -i_1 = 3 \text{ A}$$

$$R_{eq} = R_{Th} = \frac{v_o}{i_o} = \frac{1}{3} \Omega \quad \tau = \frac{L}{R_{eq}} = \frac{1/2}{1/3} = \frac{3}{2} \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$

7

### ...Example 39

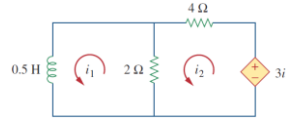

- Method 2:

$$\frac{1}{2} \frac{di_1}{dt} + 2(i_1 - i_2) = 0$$

$$\frac{di_1}{dt} + 4i_1 - 4i_2 = 0$$

$$6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$

$$\frac{di_1}{dt} + \frac{2}{3}i_1 = 0$$


$$\frac{di_1}{i_1} = -\frac{2}{3} dt \quad i_1 = i \quad \frac{di}{i} = -\frac{2}{3} dt \Rightarrow \int \frac{di}{i} = -\frac{2}{3} \int dt$$

$$\ln i \Big|_{i(0)}^{i(t)} = -\frac{2}{3} t \Big|_0^t \Rightarrow \ln \frac{i(t)}{i(0)} = -\frac{2}{3} t$$

$$i(t) = i(0)e^{-(2/3)t} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$

8

### Example 40

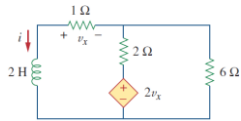


- In the circuit, if  $i(0) = 12$  A,  
- find  $i$  and  $v_x$ .

- Answer:  $12e^{-2t}$  A,  $-12e^{-2t}$  V,  $t > 0$ .


9

### Example 41...

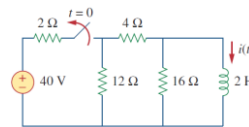

- The switch in the circuit has been closed for a long time, and it is opened at  $t = 0$ .  
- Find  $i(t)$  for  $t > 0$ .

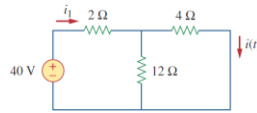- For  $t < 0$  the switch is closed; the inductor is short circuit in dc.




$$\frac{4 \times 12}{4 + 12} = 3 \Omega \quad i_1 = \frac{40}{2 + 3} = 8 \text{ A}$$

$$i(t) = \frac{12}{12 + 4} i_1 = 6 \text{ A}, \quad t < 0$$

10
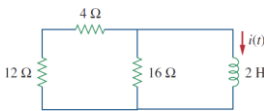
### ...Example 41

- Since the current through an inductor cannot change instantaneously,  
 $i(0) = i(0^-) = 6$  A
- For  $t > 0$  the switch is open; the voltage source is disconnected.




$$R_{eq} = (12 + 4) \parallel 16 = 8 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 6e^{-4t} \text{ A}$$

11

### Example 42

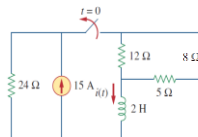


- For the circuit, find  $i(t)$  for  $t > 0$ .

- Answer:  $5e^{-2t}$  A,  $t > 0$ .

12


### Example 43...

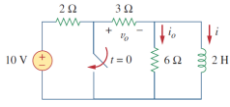

- The switch in the circuit has been open for a long time, and it is closed at  $t = 0$ .

– Find  $i_0$ ,  $v_0$ , and  $i$  for all time.

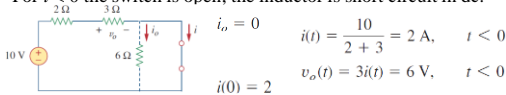
- For  $t < 0$  the switch is open; the inductor is short circuit in dc.



$$i_0 = 0 \quad i(t) = \frac{10}{2+3} = 2 \text{ A}, \quad t < 0$$

$$i(0) = 2 \quad v_0(t) = 3i(t) = 6 \text{ V}, \quad t < 0$$

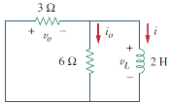- For  $t > 0$  the switch is closed; voltage source is short-circuited



$$R_{Th} = 3 \parallel 6 = 2 \Omega \quad \tau = \frac{L}{R_{Th}} = 1 \text{ s}$$

$$i(t) = i(0)e^{-t/\tau} = 2e^{-t} \text{ A}, \quad t > 0$$

13

### ...Example 43

- Since the inductor is in parallel with the 6 Ω and 3 Ω resistors,


$$v_0(t) = -v_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}, \quad t > 0$$

$$i_0(t) = \frac{v_L}{6} = -\frac{2}{3}e^{-t} \text{ A}, \quad t > 0$$

- For all time,

$$i(t) = \begin{cases} 2 \text{ A}, & t < 0 \\ 2e^{-t} \text{ A}, & t \geq 0 \end{cases}$$

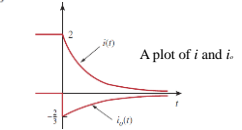
$$i_0(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ -\frac{2}{3}e^{-t} \text{ A}, & t > 0 \end{cases}$$



$$v_0(t) = \begin{cases} 6 \text{ V}, & t < 0 \\ 4e^{-t} \text{ V}, & t > 0 \end{cases}$$

14

### Example 44

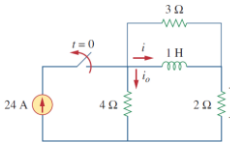


- Determine  $i$ ,  $i_0$ , and  $v_0$  for all  $t$  in the circuit shown.
- Assume that the switch was closed for a long time.
- Answer:

$$i = \begin{cases} 16 \text{ A}, & t < 0 \\ 16e^{-2t} \text{ A}, & t \geq 0 \end{cases} \quad i_0 = \begin{cases} 8 \text{ A}, & t < 0 \\ -5.333e^{-2t} \text{ A}, & t > 0 \end{cases}$$


$$v_0 = \begin{cases} 32 \text{ V}, & t < 0 \\ 10.667e^{-2t} \text{ V}, & t > 0 \end{cases}$$

15

### Example 45

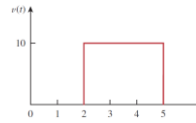


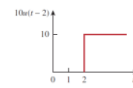- Express the voltage pulse (gate function) in terms of the unit step.
- Calculate its derivative and sketch it.




$$v(t) = 10u(t-2) - 10u(t-5) = 10[u(t-2) - u(t-5)]$$
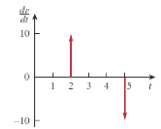
$$\frac{dv}{dt} = 10[\delta(t-2) - \delta(t-5)]$$



16

### Example 46

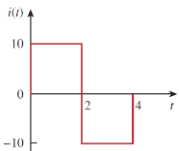


- Express the current pulse in the figure in terms of the unit step.
- Find its integral and sketch it.

- Answer:


$$10[u(t) - 2u(t-2) + u(t-4)],$$

$$10[r(t) - 2r(t-2) + r(t-4)]$$

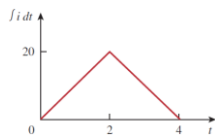


17


### Example 47...

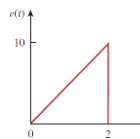

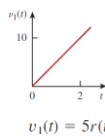
- Express the sawtooth function shown in the figure in terms of singularity functions.
- Solution 1:



$$v_1(t) = 5r(t)$$

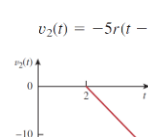

$$v_2(t) = -5r(t-2)$$

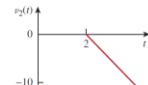


$$v_1 + v_2$$

$$5r(t) - 5r(t-2)$$

18

### ...Example 47...

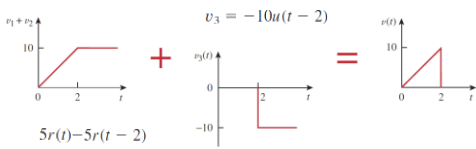

$$5r(t) - 5r(t-2)$$

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

$$v(t) = 5r(t) - 5r(t-2) - 10u(t-2)$$

19

### ...Example 47...

• Solution 2:

- $v(t)$  is a multiplication of two functions:
  - a ramp function and a gate function.


$$\begin{aligned} v(t) &= 5t[u(t) - u(t-2)] \\ &= 5tu(t) - 5tu(t-2) \\ &= 5r(t) - 5(t-2+2)u(t-2) \\ &= 5r(t) - 5(t-2)u(t-2) - 10u(t-2) \\ &= 5r(t) - 5r(t-2) - 10u(t-2) \end{aligned}$$

20
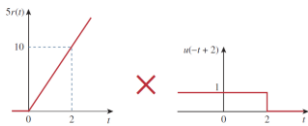
### ...Example 47

• Solution 3:

- $v(t)$  is a multiplication of two functions:
  - a ramp function and a unit step function.




$$v(t) = 5r(t)u(-t+2)$$

$$v(t) = 5r(t)[1 - u(t-2)]$$

21

### Example 48

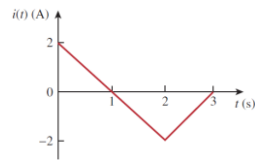

- Express  $i(t)$  in terms of singularity functions.

• Answer:

$$2u(t) - 2r(t) + 4r(t-2) - 2r(t-3) \text{ A}$$

22

### Example 49

- Express the signal  $g(t)$  in terms of step and ramp functions.

$$g(t) = \begin{cases} 3, & t < 0 \\ -2, & 0 < t < 1 \\ 2t - 4, & t > 1 \end{cases}$$

$$\begin{aligned} g(t) &= 3u(-t) - 2[u(t) - u(t-1)] + (2t-4)u(t-1) \\ &= 3u(-t) - 2u(t) + (2t-4+2)u(t-1) \\ &= 3u(-t) - 2u(t) + 2(t-1)u(t-1) \\ &= 3u(-t) - 2u(t) + 2r(t-1) \end{aligned}$$

$$g(t) = 3[1 - u(t)] - 2u(t) + 2r(t-1) = 3 - 5u(t) + 2r(t-1)$$

23

### Example 50

- Express  $h(t)$  in terms of the singularity functions.

$$h(t) = \begin{cases} 0, & t < 0 \\ -4, & 0 < t < 2 \\ 3t - 8, & 2 < t < 6 \\ 0, & t > 6 \end{cases}$$

• Answer:

$$-4u(t) + 2u(t-2) + 3r(t-2) - 10u(t-6) - 3r(t-6)$$

24

### Example 51

- Evaluate the following integrals involving the impulse function:  $\int_0^{10} (t^2 + 4t - 2)\delta(t - 2)dt$   
 $\int_{-\infty}^{\infty} [\delta(t - 1)e^{-t} \cos t + \delta(t + 1)e^{-t} \sin t]dt$

$$\int_0^{10} (t^2 + 4t - 2)\delta(t - 2)dt = (t^2 + 4t - 2)|_{t=2} = 4 + 8 - 2 = 10$$

$$\begin{aligned} \int_{-\infty}^{\infty} [\delta(t - 1)e^{-t} \cos t + \delta(t + 1)e^{-t} \sin t]dt \\ = e^{-t} \cos t|_{t=1} + e^{-t} \sin t|_{t=-1} \\ = e^{-1} \cos 1 + e^1 \sin(-1) = 0.1988 - 2.2873 = -2.0885 \end{aligned}$$

25

### Example 52

- Evaluate the following integrals:

$$\int_{-\infty}^{\infty} (t^3 + 5t^2 + 10)\delta(t + 3)dt, \quad \int_0^{10} \delta(t - \pi) \cos 3t dt$$

- Answer: 28, -1

26