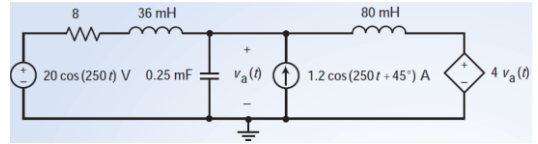


# Examples

1


## Example 53...

- Determine the voltage  $v_a(t)$  for the following circuit



2

## ...Example 53...

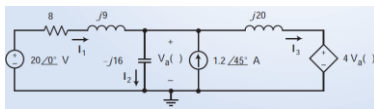


$$I_1 = \frac{20 \angle 0^\circ - V_a(\omega)}{8 - j9} \rightarrow \text{Circuit diagram showing } I_1 \text{ through the } 8 \Omega \text{ resistor and } j\beta \text{ inductor.}$$

$$I_2 = \frac{V_a(\omega) - 0}{-j16} = \frac{V_a(\omega)}{-j16} \rightarrow \text{Circuit diagram showing } I_2 \text{ through the } -j16 \text{ capacitor.}$$

$$I_3 = \frac{V_a(\omega) - 4V_a(\omega)}{j20} = -\frac{3V_a(\omega)}{j20} \rightarrow \text{Circuit diagram showing } I_3 \text{ through the } j20 \text{ inductor.}$$

3

## ...Example 53

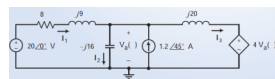

Applying KCL at the top node of the capacitor gives

$$I_1 + 1.2 \angle 45^\circ = I_2 + I_3$$

Substituting for  $I_1$ ,  $I_2$  and  $I_3$  gives

$$\frac{20 \angle 0^\circ - V_a(\omega)}{8 - j9} + 1.2 \angle 45^\circ = \frac{V_a(\omega)}{-j16} + \left( -\frac{3V_a(\omega)}{j20} \right)$$

Collecting the terms involving  $V_d(\omega)$  gives

$$\frac{20 \angle 0^\circ}{8 - j9} + 1.2 \angle 45^\circ = \left( \frac{1}{8 - j9} + \frac{1}{-j16} - \frac{3}{j20} \right) V_a(\omega)$$

Solving for  $V_a(\omega)$ , perhaps using MATLAB (see Figure 10.6-5), gives

$$V_a(\omega) = 12.43 \angle -81.2^\circ \text{ V}$$


The corresponding sinusoid is

$$v_a(t) = 12.43 \cos(250t - 81.2^\circ) \text{ V}$$

4
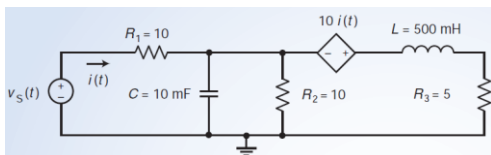
## Example 54...

- Input to the circuit is the voltage source voltage  $v_s(t) = 10 \cos(10t)$  V.
- The output is the current  $i(t)$  in resistor  $R_1$ .
- Determine  $i(t)$ .



5


## ...Example 54...

First, we will represent the circuit in the frequency domain using phasors and impedances. The impedances of the capacitor and inductor are

$$Z_c = -j \frac{1}{10(0.010)} = -j10 \Omega \text{ and } Z_l = j10(0.5) = j5 \Omega$$


The frequency domain representation of the circuit is shown in Figure . We can analyze this circuit by writing and solving node equations. To simplify this process, we can first replace series and parallel impedances by equivalent impedances as shown in Figure . Impedances  $Z_1$  and  $Z_2$  in Figure are given by
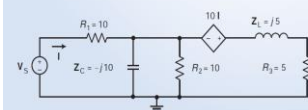
$$Z_1 = 10 \parallel (-j10) = \frac{10(-j10)}{10 - j10} = 5 - j5 \Omega \text{ and } Z_2 = 5 + j5 \Omega$$



6

### ...Example 54

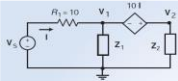

Next, consider the dependent source in Figure . We can use Ohm's law to express the controlling current  $I$  as

$$I = \frac{V_2 - V_1}{R_1}$$

Using KVL, we can express the dependent source voltage as

$$10I = V_2 - V_1$$

Apply KCL to the supernode identified in Figure to get

$$I = \frac{V_1}{Z_2} + \frac{V_2}{Z_3} = \frac{V_1 + 10I}{Z_2} \Rightarrow (Z_2 + Z_3)V_1 + Z_2(10 - Z_3)I = 0$$

Organizing Eqs. into matrix form, we get

$$\begin{bmatrix} 1 & R_1 \\ Z_2 + Z_3 & Z_2(10 - Z_3) \end{bmatrix} \begin{bmatrix} V_1 \\ I \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

Solving these equations, perhaps using MATLAB, gives

$$V_1 = 4.4721 \angle 63.4^\circ \text{ V and } I = 0.89443 \angle -26.6^\circ \text{ A}$$


Back in the time domain, the output current is

$$i(t) = 0.89443 \cos(10t - 26.6^\circ) \text{ A}$$

7
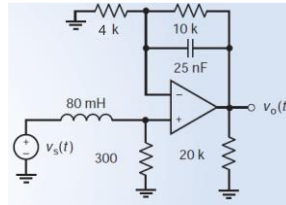
### Example 55...

- Input to the circuit is the voltage source voltage  $v_s(t) = 125 \cos(500t + 15^\circ) \text{ mV}$ .



- Determine the output voltage  $i(t)$ .


8

### ...Example 55...

The impedances of the capacitor and inductor are

$$Z_C = -j \frac{1}{5000(25 \times 10^{-9})} = -j8000 \Omega \text{ and } Z_L = j5000(80 \times 10^{-3}) = j400 \Omega$$

Figure show the circuit represented in the frequency domain using phasors and impedances.

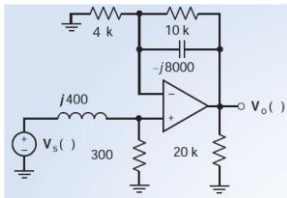

9

### ...Example 55

Applying KCL at the noninverting node of the op amp, we get

$$\frac{V_s - V_1}{4000} = \frac{V_1 - V_o}{300} + 0 \Rightarrow V_s = V_1 \left( 1 + \frac{j400}{300} \right)$$

Solving for  $V_a$  gives

$$V_a = \left( \frac{300}{300 + j400} \right) V_s = (0.6 \angle -53.1^\circ) (0.125 \angle 15^\circ) = 0.075 \angle -38.1^\circ \text{ V}$$

Next, apply KCL at the inverting node of the op amp to get

$$\frac{V_a}{4000} + \frac{V_a - V_o}{10,000} + \frac{V_a - V_o}{-j8000} = 0$$

Multiplying by 80,000 gives

$$0 = 20V_a + 8(V_a - V_o) + j10(V_a - V_o)$$

Solving for  $V_o$  gives

$$V_o = \frac{28 + j10}{8 + j10} V_a = \frac{29.73 \angle 19.65^\circ}{12.81 \angle 51.34^\circ} (0.075 \angle -38.1^\circ) = 0.174 \angle -69.79^\circ$$


In the time domain, the output voltage is

$$v_o(t) = 174 \cos(500t - 69.79^\circ) \text{ mV}$$

10
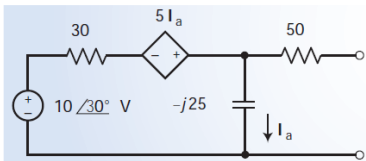
### Example 56...

- Find the Norton equivalent circuit of the following ac circuit.



11

### ...Example 56...

In Figure an open circuit is connected across the terminals of circuit. The voltage across that open circuit is the open-circuit voltage  $V_{oc}$ . (Notice that there is no current in the 50-ohm impedance due to the open circuit.) Apply KVL to the left mesh to get


$$30I_a - 5I_a + (-j25)I_a = 10 \angle 30^\circ$$

Solving for  $I_a$  we get

$$I_a = \frac{10 \angle 30^\circ}{25 - j25} = 0.2828 \angle 25^\circ \text{ A}$$

Apply KVL to the right mesh to get
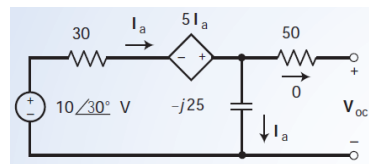
$$V_{oc} = -j25I_a = (25 \angle -90^\circ)(0.2828 \angle 25^\circ) = 7.071 \angle -15^\circ \text{ V}$$



12

### ...Example 56...

Next, we determine the short-circuit current using the circuit shown in Figure 10.7.9. In Figure 10.7.9, a short circuit is connected across the terminals of circuit. The current in that open circuit is the short-circuit current  $I_{sc}$ . In Figure 10.7.9, the controlling current of the dependent source is related to the mesh currents by

$$I_x = I_1 - I_{sc}$$

Apply KVL to the left mesh to get

$$30I_1 - 5(I_1 - I_{sc}) - j25(I_1 - I_{sc}) = 10\angle 30^\circ$$

Apply KVL to the right mesh to get


$$50I_{sc} - (-j25)(I_1 - I_{sc}) = 0$$

Organize these equations in matrix form to get

$$\begin{bmatrix} 25 - j25 & 5 + j25 \\ j25 & 50 - j25 \end{bmatrix} \begin{bmatrix} I_1 \\ I_{sc} \end{bmatrix} = \begin{bmatrix} 10\angle 30^\circ \\ 0 \end{bmatrix}$$

Solving using MATLAB gives
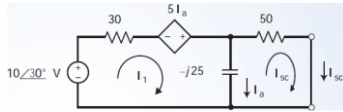
$$\begin{bmatrix} I_1 \\ I_{sc} \end{bmatrix} = \begin{bmatrix} 0.2370\angle 61.4^\circ \\ 0.1060\angle -2^\circ \end{bmatrix}$$




13

### ...Example 56

The Thévenin impedance is

$$Z_t = \frac{V_{oc}}{I_{sc}} = \frac{7.071\angle -15^\circ}{0.1060\angle -2^\circ} = 66.71\angle -13^\circ \Omega$$

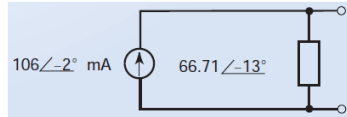Finally, Figure 10.7.10 shows the Norton equivalent circuit, which consists of a current source in parallel with an impedance. The current source current is the short-circuit voltage  $I_{sc}$ . The impedance is the Thévenin impedance  $Z_t$ .



14