

the equations will reveal that the isolation provided by the JFET between the gate and channel by the SiO₂ layer results in a series of less complex equations than those encountered for the BJT configurations. The linkage provided by I_b between input and output circuits of the BJT transistor amplifier adds a touch of complexity to some of the equations.

TABLE 10.1 Summary of Transistor Configurations (A_v , Z_i , Z_o)			
Configuration	$A_v = V_o/V_i$	Z_i	Z_o
	$\frac{-R_L \parallel R_C}{r_e}$ $\frac{-h_{fe}}{h_{ie}}(R_L \parallel R_C)$ Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_B \parallel \beta r_e$ $R_B \parallel h_{ie}$	R_C R_C $R_C \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{r_e}$ $\frac{-h_{fe}}{h_{ie}}(R_L \parallel R_C)$ Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_1 \parallel R_2 \parallel \beta r_e$ $R_1 \parallel R_2 \parallel h_{ie}$	R_C R_C $R_C \parallel r_o$
	$\cong 1$ $\cong 1$ Including r_o : $\cong 1$	$R'_E = R_L \parallel R_E$ $R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$ $R_1 \parallel R_2 \parallel (h_{ie} + h_{fe}R'_E)$	$R'_s = R_s \parallel R_1 \parallel R_2$ $R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right)$ $R_E \parallel \left(\frac{R'_s + h_{ie}}{h_{fe}} \right)$
	$\cong \frac{-(R_L \parallel R_C)}{r_e}$ $\cong \frac{-h_{fb}}{h_{ib}}(R_L \parallel R_C)$ Including r_o : $\cong \frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_E \parallel r_e$ $R_E \parallel h_{ib}$	R_C R_C $R_C \parallel r_o$

TABLE 10.1 Summary of Transistor Configurations (A_v , Z_i , Z_o) (Continued)

Configuration	$A_v = V_o/V_i$	Z_i	Z_o
	$\frac{-R_L \parallel R_C}{R_E}$ $\frac{-(R_L \parallel R_C)}{R_E}$ Including r_o : $\frac{-(R_L \parallel R_C)}{R_E}$	$R_1 \parallel R_2 \parallel \beta(r_e + R_E)$ $R_1 \parallel R_2 \parallel (h_{ie} + h_{fe}R_E)$ $R_1 \parallel R_2 \parallel \beta(r_e + R_E)$	R_C R_C $\cong R_C$
	$\frac{-R_L \parallel R_C}{R_{E1}}$ $\frac{-(R_L \parallel R_C)}{R_{E1}}$ Including r_o : $\frac{-R_L \parallel R_C}{R_{E1}}$	$R_B \parallel \beta(r_e + R_{E1})$ $R_B \parallel (h_{ie} + h_{fe}R_{E1})$ $R_B \parallel \beta(r_e + R_{E1})$	R_C R_C $\cong R_C$
	$\frac{-(R_L \parallel R_C)}{r_e}$ $\frac{-h_{fe}}{h_{ie}}(R_L \parallel R_C)$ Including r_o : $\frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$\beta r_e \parallel \frac{R_F}{ A_v }$ $h_{ie} \parallel \frac{R_F}{ A_v }$ $\beta r_e \parallel \frac{R_F}{ A_v }$	R_C R_C $R_C \parallel R_F \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{R_E}$ $\frac{-(R_L \parallel R_C)}{R_E}$ Including r_o : $\cong \frac{-(R_L \parallel R_C)}{R_E}$	$\beta R_E \parallel \frac{R_F}{ A_v }$ $h_{fe} R_E \parallel \frac{R_F}{ A_v }$ $\cong \beta R_E \parallel \frac{R_F}{ A_v }$	$\cong R_C \parallel R_F$ $\cong R_C \parallel R_F$ $\cong R_C \parallel R_F$

TABLE 10.1 (Continued)

Configuration	$A_v = V_o/V_i$	Z_i	Z_o
	$-g_m(R_D \parallel R_L)$ Including r_d : $-g_m(R_D \parallel R_L \parallel r_d)$	R_G R_G	R_D $R_D \parallel r_d$
	$\frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S}$ Including r_d : $\frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$	R_G R_G	$\frac{R_D}{1 + g_m R_S}$ $\cong \frac{R_D}{1 + g_m R_S}$
	$-g_m(R_D \parallel R_L)$ Including r_d : $-g_m(R_D \parallel R_L \parallel r_d)$	$R_1 \parallel R_2$ $R_1 \parallel R_2$	R_D $R_D \parallel r_d$
	$\frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)}$ Including r_d : $= \frac{g_m r_d (R_S \parallel R_L)}{r_d + R_D + g_m r_d (R_S \parallel R_L)}$	R_G R_G	$R_S \parallel 1/g_m$ $\frac{R_S}{1 + \frac{g_m r_d R_S}{r_d + R_D}}$
	$g_m(R_D \parallel R_L)$ Including r_d : $\cong g_m(R_D \parallel R_L)$	$\frac{R_S}{1 + g_m R_S}$ $Z_i = \frac{R_S}{1 + \frac{g_m r_d R_S}{r_d + R_D \parallel R_L}}$	R_D $R_D \parallel r_d$