

Electronic Circuits

Prof. Dr. Nizamettin AYDIN

naydin@yildiz.edu.tr

<http://www.yildiz.edu.tr/~naydin>

1

Operational amplifiers


- Introduction
- An ideal operational amplifier
- Basic operational amplifier circuits
- Other useful circuits
- Real operational amplifiers
- Selecting component values
- Effects of feedback on op-amp circuits

2

Introduction...

- Operational amplifiers (op-amps) are among the most widely used building blocks in electronics


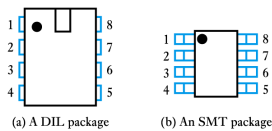
- they are integrated circuits (ICs)
- often DIL or SMT



3


...Introduction

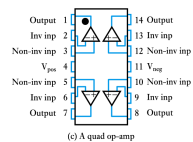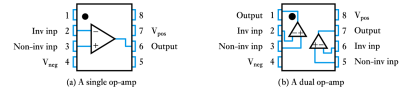- A single package will often contain several op-amps



4


Inside the Op-Amp (IC-chip)

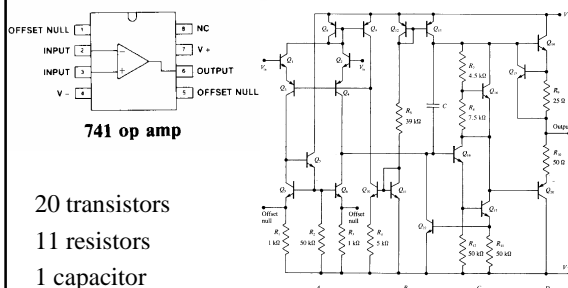

5

Ideal Op-Amp

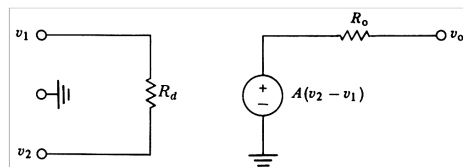
- Most bioelectric signals are small and require amplifications
- Op-amp equivalent circuit:**



The two inputs are v_1 and v_2 . A differential voltage between them causes current flow through the differential resistance R_d . The differential voltage is multiplied by A , the gain of the op amp, to generate the output-voltage source. Any current flowing to the output terminal v_o must pass through the output resistance R_o .

6


Ideal Characteristics

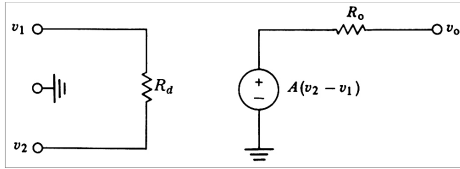

- $A = \infty$ (gain is infinity)
- $V_o = 0$, when $v_1 = v_2$ (no offset voltage)
- $R_d = \infty$ (input impedance is infinity)
- $R_o = 0$ (output impedance is zero)
- Bandwidth = ∞ (no frequency response limitations) and no phase shift

7

Two Basic Rules

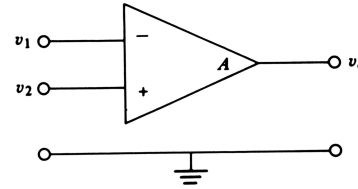


- **Rule 1**
 - When the op-amp output is in its linear range, the two input terminals are at the same voltage.
- **Rule 2**
 - No current flows into or out of either input terminal of the op amp.

8

Basic operational amplifier circuits...

- Inverting and non-inverting amplifiers

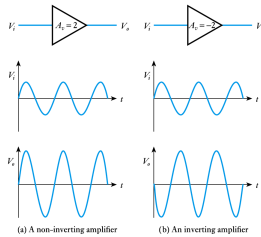

9

...Basic operational amplifier circuits...

- When looking at feedback we derived the circuit of an amplifier from 'first principles'
- Normally we use standard 'cookbook' circuits and select component values to suit our needs
- In analysing these we normally assume the use of ideal op-amps
 - in demanding applications we may need to investigate the appropriateness of this assumption
 - the use of ideal components makes the analysis of these circuits very straightforward

10

...Basic operational amplifier circuits...

- A non-inverting amplifier

Analysis

Since the gain is assumed infinite, if V_o is finite then the input voltage must be zero. Hence $V_- = V_+ = V_i$

Since the input resistance of the op-amp is ∞


$$V_- = V_o \frac{R_2}{R_1 + R_2}$$

and hence, since $V_- = V_+ = V_i$

$$V_i = V_o \frac{R_2}{R_1 + R_2}$$

and
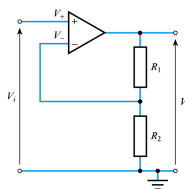
$$G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$$



11

...Basic operational amplifier circuits...

- Example

Design a non-inverting amplifier with a gain of 25

From above $G = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2}$


If $G = 25$ then

$$\frac{R_1 + R_2}{R_2} = 25$$

$$R_1 + R_2 = 25 R_2$$

$$R_1 = 24 R_2$$

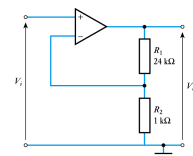Therefore choose $R_2 = 1 \text{ k}\Omega$ and $R_1 = 24 \text{ k}\Omega$ (choice of values will be discussed later)



12

...Basic operational amplifier circuits...


- An inverting amplifier

Analysis...

Since the gain is assumed infinite, if V_o is finite the input voltage must be zero. Hence $V_- = V_+ = 0$

Since the input resistance of the op-amp is ∞ its input current must be zero, and hence
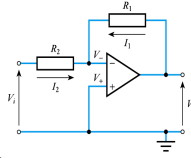
$$\text{Now } I_1 = \frac{V_o - V_-}{R_1} = \frac{V_o - 0}{R_1} = \frac{V_o}{R_1} \quad I_2 = \frac{V_i - V_-}{R_2} = \frac{V_i - 0}{R_2} = \frac{V_i}{R_2}$$



13

...Basic operational amplifier circuits...

...Analysis


Therefore, since $I_1 = -I_2$

$$\frac{V_o}{R_1} = -\frac{V_i}{R_2}$$

or, rearranging

$$G = \frac{V_o}{V_i} = -\frac{R_1}{R_2}$$

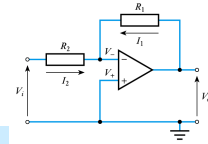- Here V_- is held at zero volts by the operation of the circuit, hence the circuit is known as a **virtual earth circuit**



14

...Basic operational amplifier circuits

- Example

Design an inverting amplifier with a gain of -25

From above


$$G = \frac{V_o}{V_i} = -\frac{R_1}{R_2}$$

If $G = -25$ then

$$-\frac{R_1}{R_2} = -25$$

$$R_1 = 25R_2$$

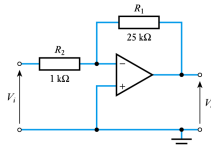Therefore choose $R_2 = 1 \text{ k}\Omega$ and $R_1 = 25 \text{ k}\Omega$ (we will consider the choice of values later)



15

Other useful circuits...

- In addition to simple amplifiers, op-amps can also be used in a range of other circuit
- The next few slides show a few examples of op-amp circuits for a range of purposes
- The analysis of these circuits is similar to that of the non-inverting and inverting amplifiers but (in most cases) this is *not* included here
- For more details of these circuits see the relevant section of the course text (as shown on the slides)

16

...Other useful circuits...

- A unity gain buffer amplifier

Analysis


This is a special case of the non-inverting amplifier with $R_1 = 0$ and $R_2 = \infty$

Hence

$$G = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + 1 = \frac{0}{\infty} + 1 = 1$$

Thus the circuit has a gain of unity

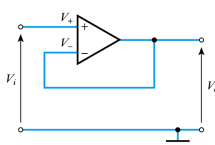
- At first sight this might not seem like a very useful circuit, however, it has a high input resistance and a low output resistance and is therefore useful as a **buffer amplifier**



17

...Other useful circuits...

- A current to voltage converter

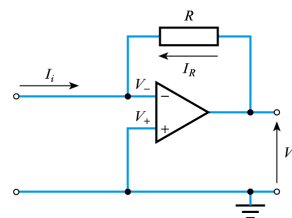


$$V_o = -I_i R$$

18

...Other useful circuits...

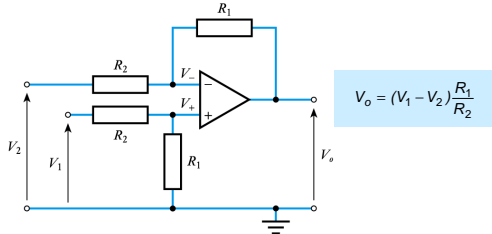- A differential amplifier (or subtractor)




$$V_o = (V_1 - V_2) \frac{R_1}{R_2}$$

19

...Other useful circuits...

- An inverting summing amplifier

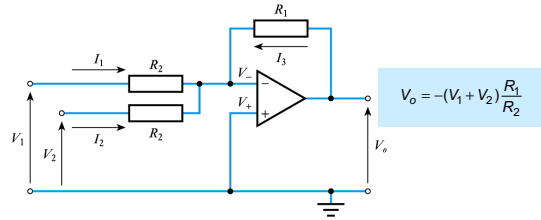


$$V_o = -(V_1 + V_2) \frac{R_1}{R_2}$$

20

...Other useful circuits...

- An integrator

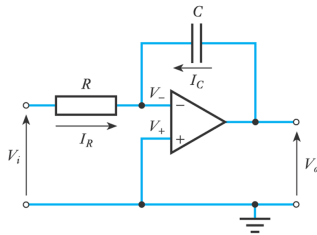


$$V_o = -\frac{1}{RC} \int_0^t V_i dt$$

21

...Other useful circuits


- A differentiator

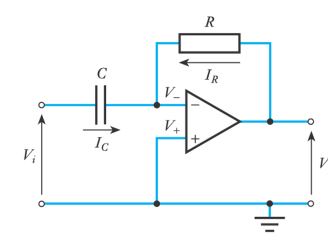

$$V_o = -RC \frac{dV_i}{dt}$$

22

Display Driver

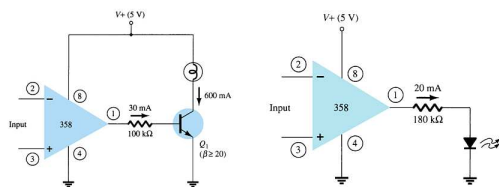

23

Differential Amplifiers

- Differential Gain G_d


$$G_d = \frac{v_o}{v_4 - v_3} = \frac{R_4}{R_3}$$

- Common Mode Gain G_c

- For ideal op amp if the inputs are equal then the output = 0, and the $G_c = 0$.
- No differential amplifier perfectly rejects the common-mode voltage.

- Common-mode rejection ratio $CMMR$

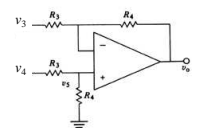- Typical values range from 100 to 10,000




$$v_o = \frac{R_4}{R_3} (v_4 - v_3)$$

$$CMMR = \frac{G_d}{G_c}$$

- Disadvantage of one-op-amp differential amplifier is its low input resistance

24

Instrumentation Amplifiers

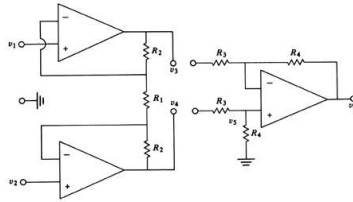

Differential Mode Gain

$$v_3 - v_4 = i(R_2 + R_1 + R_2)$$

$$v_1 - v_2 = iR_1$$

$$G_d = \frac{v_3 - v_4}{v_1 - v_2} = \frac{2R_2 + R_1}{R_1}$$


Advantages: High input impedance, High CMRR, Variable gain

25

Active Filters

Adding capacitors to op-amp circuits provides external control of the cutoff frequencies. The op-amp active filter provides controllable cutoff frequencies and controllable gain.

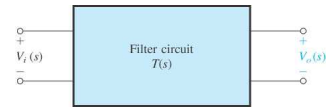
- Low-pass filter
- High-pass filter
- Bandpass filter
- Bandstop filter



The filter transfer function $T(s) \equiv V_o(s)/V_i(s)$.


26

Ideal transmission characteristics

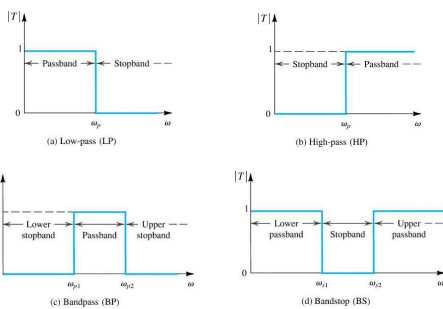


27

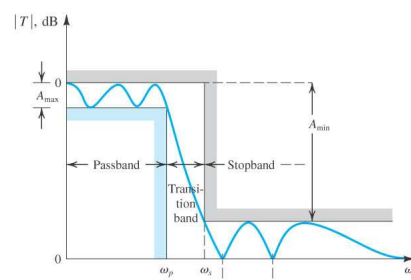Specification of the transmission characteristics of a low-pass filter




28

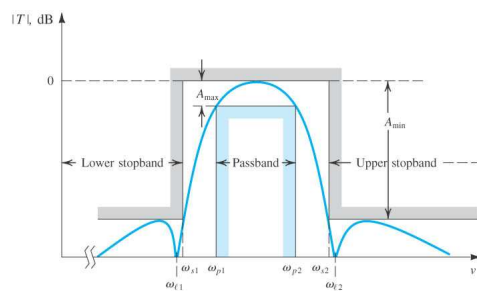Specification of the transmission characteristics of a bandpass filter



29

Low-Pass Filter—First-Order

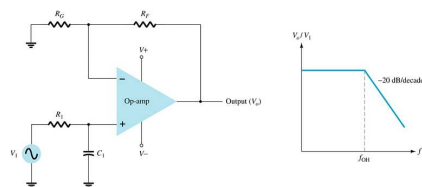


The upper cutoff frequency and voltage gain are given by:

$$f_{0H} = \frac{1}{2\pi R_1 C_1} \quad A_v = 1 + \frac{R_f}{R_1}$$

30


Low-Pass Filter—Second-Order

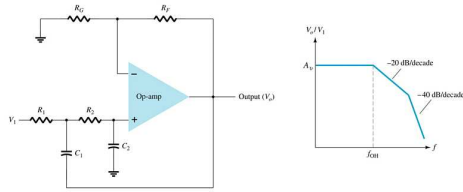

The roll-off can be made steeper by adding more RC networks.

31

High-Pass Filter

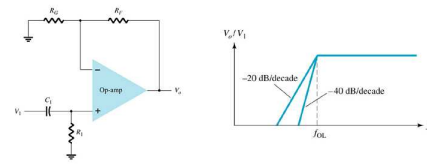



The cutoff frequency is determined by:

$$f_{OL} = \frac{1}{2\pi R_1 C_1}$$

32

Bandpass Filter

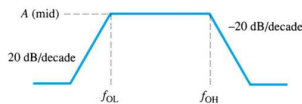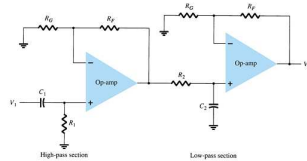There are two cutoff frequencies: upper and lower. They can be calculated using the same low-pass cutoff and high-pass cutoff frequency formulas in the appropriate sections.



33

Multiple-Stage Gains...

The total gain (3-stages) is given by:


$$A = A_1 A_2 A_3$$

or

$$A = \left(1 + \frac{R_f}{R_1}\right) \left(-\frac{R_f}{R_2}\right) \left(-\frac{R_f}{R_3}\right)$$

34

...Multiple-Stage Gains

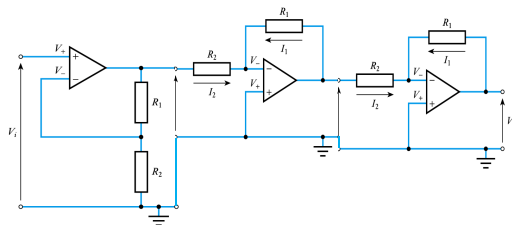

$$A_1 = \frac{V_2}{V_1} = \frac{R_1 + R_2}{R_2}$$

$$A_2 = \frac{V_3}{V_2} = -\frac{R_1}{R_2}$$

$$A_3 = \frac{V_4}{V_3} = -\frac{R_1}{R_2}$$

$$A = A_1 \times A_2 \times A_3 = \frac{R_1 + R_2}{R_2} \times \left(-\frac{R_1}{R_2}\right) \times \left(-\frac{R_1}{R_2}\right) = \frac{R_1^2 + R_1^2 \times R_2}{R_2^3}$$

35

Real operational amplifiers...

- So far we have assumed the use of **ideal op-amps**
 - these have $A_v = \infty$, $R_i = \infty$ and $R_o = 0$
- Real components do not have these ideal characteristics (though in many cases they approximate to them)
- In this section we will look at the characteristics of typical devices
 - perhaps the most widely used general purpose op-amp is the 741

36

...Real operational amplifiers...

- Voltage gain
 - typical gain of an operational amplifier might be 100 – 140 dB (voltage gain of 10^5 – 10^6)
 - 741 has a *typical* gain of 106 dB (2×10^5)
 - high gain devices might have a gain of 160 dB (10^8)
 - while not infinite, the gain of most op-amps is ‘high-enough’
 - however, gain varies between devices and with temperature

37

...Real operational amplifiers...

- Input resistance
 - typical input resistance of a 741 is $2 \text{ M}\Omega$
 - very variable, for a 741 it can be as low as $300 \text{ k}\Omega$
 - the above value is typical for devices based on **bipolar transistors**
 - op-amps based on **field-effect transistors** generally have a much higher input resistance – perhaps $10^{12} \Omega$
 - we will discuss bipolar and field-effect transistors later

38

...Real operational amplifiers...

- Output resistance
 - typical output resistance of a 741 is 75Ω
 - again very variable
 - often of more importance, is the maximum output current
 - the 741 will supply 20 mA
 - high-power devices may supply 1 ampere or more

39

...Real operational amplifiers...

- Supply voltage range
 - a typical arrangement would use supply voltages of +15 V and – 15 V, but a wide range of supply voltages is usually possible
 - the 741 can use voltages in the range ± 5 to ± 18 V
 - some devices allow voltages up to ± 30 V or more
 - others, designed for low voltages, may use ± 1.5 V
 - many op-amps permit single voltage supply operation, typically in the range 4 to 30 V

40


...Real operational amplifiers...

- Common-mode rejection ratio
 - an ideal op-amp would not respond to common-mode signals.
 - real amplifiers do respond to some extent
 - the common-mode rejection ratio (CMRR) is the ratio of the response produced by a differential-mode signal to that produced by a common-mode signal
 - typical values for CMRR might be in the range 80 to 120 dB
 - 741 has a CMRR of about 90 dB

41

...Real operational amplifiers

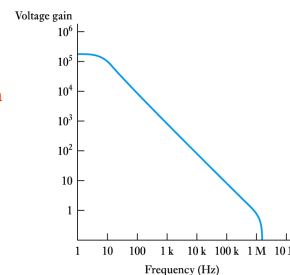- Frequency response
 - typical 741 frequency response is shown here
 - upper cut-off frequency is a few hertz
 - frequency range generally described by the **unity-gain bandwidth**
 - high-speed devices may operate up to several gigahertz



42

Selecting component values

- Our analysis assumed the use of an ideal op-amp
- When using real components we need to ensure that our assumptions are valid
- In general this will be true if we:
 - limit the gain of our circuit to *much less* than the open-loop gain of our op-amp
 - choose external resistors that are *small* compared with the input resistance of the op-amp
 - choose external resistors that are *large* compared with the output resistance of the op-amp.
- Generally we use resistors in the range 1 to 100 k Ω

43

Effects of feedback on op-amp circuits...


- Effects of feedback on the Gain
 - negative feedback *reduces* gain from A to $A/(1 + AB)$
 - in return for this loss of gain we get consistency, provided that the open-loop gain is much greater than the closed-loop gain (that is, $A \gg 1/B$)
 - using negative feedback, standard cookbook circuits can be used – greatly simplifying the design
 - these can be analysed without a detailed knowledge of the op-amp itself

44

...Effects of feedback on op-amp circuits...

- Effects of feedback on frequency response

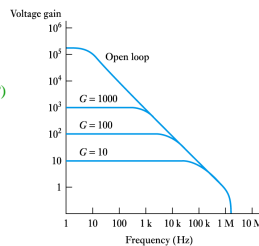- as the gain is *reduced* the bandwidth is *increased*
- gain \times bandwidth \approx constant
 - since gain is *reduced* by $(1 + AB)$ bandwidth is *increased* by $(1 + AB)$
- for a 741, gain \times bandwidth $\approx 10^6$
 - if gain = 1000 BW \approx 1000 Hz
 - if gain = 100 BW \approx 10,000 Hz



45

...Effects of feedback on op-amp circuits...

- Effects of feedback on input and output resistance

- input/output resistance can be increased or decreased depending on how feedback is used.
 - we looked at this in an earlier lecture
 - in each case the resistance is changed by a factor of $(1 + AB)$

Example

- if an op-amp with a gain of 2×10^5 is used to produce an amplifier with a gain of 100 then:

$$A = 2 \times 10^5$$

$$B = 1/G = 0.01$$


$$(1 + AB) = (1 + 2000) \approx 2000$$

46

...Effects of feedback on op-amp circuits...

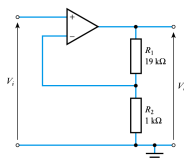- Example

- determine the input and output resistance of the following circuit assuming op-amp is a 741




Open-loop gain (A) of a 741 is 2×10^5
 Closed-loop gain ($1/B$) is 20, $B = 1/20 = 0.05$
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$
 Feedback senses **output voltage** therefore it **reduces** output resistance of op-amp (75 Ω) by 10^4 to give 7.5 m Ω
 Feedback subtracts a **voltage** from the input, therefore it **increases** the input resistance of the op-amp (2 M Ω) by 10^4 to give 20 G Ω

47

...Effects of feedback on op-amp circuits

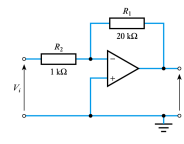- Example

- determine the input and output resistance of the following circuit assuming op-amp is a 741



Open-loop gain (A) of a 741 is 2×10^5
 Closed-loop gain ($1/B$) is 20, $B = 1/20 = 0.05$
 $(1 + AB) = (1 + 2 \times 10^5 \times 0.05) = 10^4$
 Feedback senses **output voltage** therefore, it **reduces** output resistance of op-amp (75 Ω) by 10^4 to give 7.5 m Ω
 Feedback subtracts a **current** from the input, therefore it **decreases** the input resistance. In this case the input sees R_2 to a virtual earth, therefore the input resistance is 1 k Ω

48

Key points

- Operational amplifiers are among the most widely used building blocks in electronic circuits
- An *ideal* operational amplifier would have infinite voltage gain, infinite input resistance and zero output resistance
- Designers often make use of cookbook circuits
- Real op-amps have several non-ideal characteristics. However, if we choose components appropriately this should not affect the operation of our circuits
- Feedback allows us to increase bandwidth by trading gain against bandwidth
- Feedback also allows us to alter other circuit characteristics

49