

## Electronic Circuits

Prof. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

[gokhanb@ce.yildiz.edu.tr](mailto:gokhanb@ce.yildiz.edu.tr)

1


## Transistor Construction

There are two types of transistors:

- *pnp*
- *npn*

The terminals are labeled:

- E - Emitter
- B - Base
- C - Collector

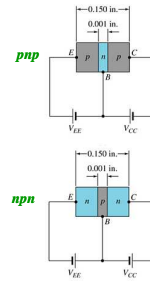


2
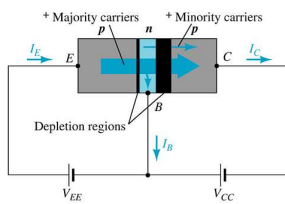
## Transistor Operation

With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:

- The emitter-base junction is forward biased
- The base-collector junction is reverse biased



3


## Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$


The collector current is comprised of two currents:
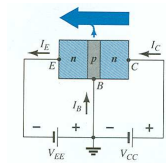
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



4

## Common-Base Configuration

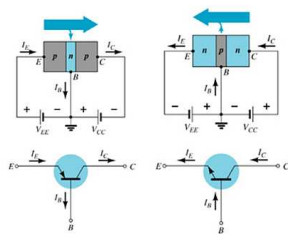


The base is common to both input (emitter-base) and output (collector-base) of the transistor.

5

## Common-Base Amplifier
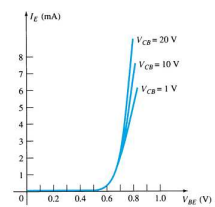
### Input Characteristics

This curve shows the relationship between input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.




6

## Common-Base Amplifier
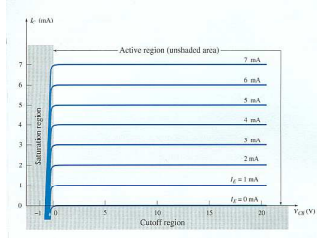
### Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).



7

## Operating Regions

- **Active** – Operating range of the amplifier.
- **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- **Saturation** – The amplifier is full on. There is current, but little voltage.

8

## Approximations

Emitter and collector currents:

$$I_C \cong I_E$$

Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

9

## Alpha ( $\alpha$ )

Alpha ( $\alpha$ ) is the ratio of  $I_C$  to  $I_E$  :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Ideally:  $\alpha = 1$


In reality:  $\alpha$  is between 0.9 and 0.998

Alpha ( $\alpha$ ) in the AC mode:

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

10

## Transistor Amplification

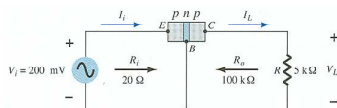

Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200\text{mV}}{20\Omega} = 10\text{mA}$$

$$I_C \cong I_E$$

$$I_L \cong I_i = 10\text{mA}$$

$$V_L = I_L R = (10\text{mA})(5\text{k}\Omega) = 50\text{V}$$

Voltage Gain:


$$A_v = \frac{V_L}{V_i} = \frac{50\text{V}}{200\text{mV}} = 250$$

11
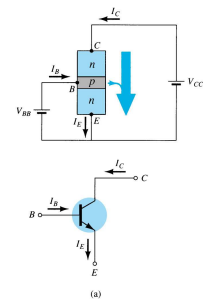
## Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).

The input is on the base and the output is on the collector.



12

## Common-Emitter Characteristics

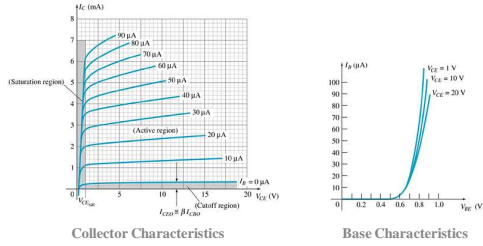

13

## Common-Emitter Amplifier Currents

### Ideal Currents

$$I_E = I_C + I_B \quad I_C = \alpha I_E$$

### Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

$I_{CBO}$  is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When  $I_B = 0 \mu\text{A}$  the transistor is in cutoff, but there is some minority current flowing called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \quad I_B = 0 \mu\text{A}$$

14

## Beta ( $\beta$ )

$\beta$  represents the amplification factor of a transistor. ( $\beta$  is sometimes referred to as  $h_{fe}$ , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

In AC mode:

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \bigg|_{V_{CE} = \text{constant}}$$


15

## Beta ( $\beta$ )

Determining  $\beta$  from a Graph

$$\beta_{AC} = \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu\text{A} - 20 \mu\text{A})} = \frac{1 \text{ mA}}{10 \mu\text{A}} \bigg|_{V_{CE} = 7.5} = 100$$

$$\beta_{DC} = \frac{2.7 \text{ mA}}{25 \mu\text{A}} \bigg|_{V_{CE} = 7.5} = 108$$

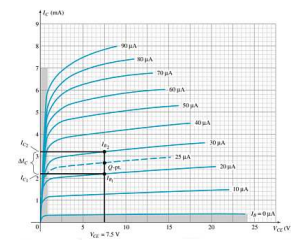

16

## Beta ( $\beta$ )

Relationship between amplification factors  $\beta$  and  $\alpha$

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B \quad I_E = (\beta + 1) I_B$$

17
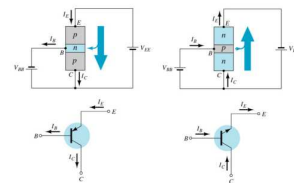
## Common-Collector Configuration


The input is on the base and the output is on the emitter.



18
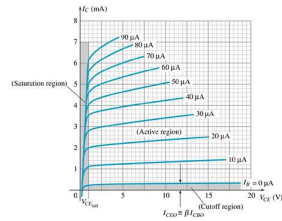
## Common-Collector Configuration

The characteristics are similar to those of the common-emitter configuration, except the vertical axis is  $I_E$ .




19

## Operating Limits for Each Configuration

$V_{CE}$  is at maximum and  $I_C$  is at minimum ( $I_{Cmax} = I_{CE0}$ ) in the cutoff region.

$I_C$  is at maximum and  $V_{CE}$  is at minimum ( $V_{CEmax} = V_{CEsat} = V_{CE0}$ ) in the saturation region.

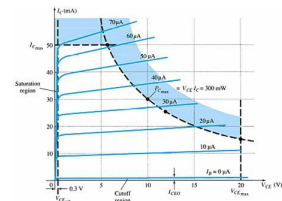The transistor operates in the active region between saturation and cutoff.



20

## Power Dissipation

Common-base:

$$P_{Cmax} = V_{CB} I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE} I_C$$

Common-collector:

$$P_{Cmax} = V_{CE} I_E$$

21

## Transistor Specification Sheet

### MAXIMUM RATINGS

Rating Symbol 2N4123 Unit

Collector-Emitter Breakdown Voltage  $V_{CE0}$  30 Vdc

Collector-Base Voltage  $V_{CB0}$  30 Vdc

Emitter-Base Voltage  $V_{EB0}$  5.0 Vdc

Collector Current - Continuous  $I_C$  200 mAdc

Total Device Dissipation at  $T_C = 25^\circ\text{C}$   $P_D$  625 mW

Dissip above  $25^\circ\text{C}$  5.0 mW/°C

Operating and Storage Junction Temperature Range  $T_J, T_{stg}$  -55 to +150 °C

Operating and Storage Junction Temperature Range

Thermal Resistance, Junction to Case  $R_{\theta jc}$  33.3 °C/W

Thermal Resistance, Junction to Ambient  $R_{\theta ja}$  200 °C/W

Thermal Resistance, Junction to Ambient



Thermal Resistance, Junction to Case

Thermal Resistance, Junction to Ambient

Thermal Resistance, Junction to Ambient

Thermal Resistance, Junction to Ambient

Thermal Resistance, Junction to Ambient

22

## Transistor Specification Sheet

Characteristics	Symbol	Min	Max	Unit
<b>OFF CHARACTERISTICS</b>				
Collector-Emitter Breakdown Voltage (1)	$V_{CE0}$	30	—	Vdc
Collector-Base Breakdown Voltage (1)	$V_{CB0}$	30	—	Vdc
Emitter-Base Breakdown Voltage (1)	$V_{EB0}$	5.0	—	Vdc
Collector Current - Continuous (1)	$I_C$	—	200	mAdc
Emitter Current - Continuous (1)	$I_E$	—	200	mAdc
Base Current - Continuous (1)	$I_B$	—	50	mAdc
<b>ON CHARACTERISTICS</b>				
DC Current Gain (1)	$\beta_{DC}$	20	150	—
Collector-Emitter Saturation Voltage (1)	$V_{CE(sat)}$	—	0.3	Vdc
Base-Emitter Saturation Voltage (1)	$V_{BE(sat)}$	—	0.65	Vdc
<b>SMALL-SIGNAL CHARACTERISTICS</b>				
Current Gain - Breakdown Point (1)	$\beta_{DC}$	20	—	dBdc
Output Capacitance (1)	$C_{out}$	—	4.0	pF
Input Capacitance (1)	$C_{in}$	—	8.0	pF
Collector-Base Capacitance (1)	$C_{cb}$	—	4.0	pF
Small-Signal Current Gain (1)	$\beta_{AC}$	30	200	—
Current Gain - High Frequency (1)	$\beta_{AC}$	2.0	—	—
Noise Figure (1)	NF	—	6.0	dB


23

## Transistor Testing

- Curve Tracer  
Provides a graph of the characteristic curves.


- DMM  
Some DMMs measure  $\beta_{DC}$  or  $h_{FE}$ .

- Ohmmeter

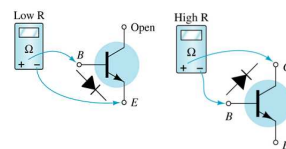

24

## Transistor Terminal Identification

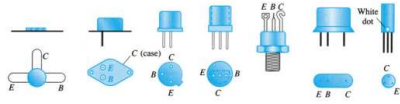

25