

## Electronic Circuits

Prof. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin


[gokhanb@ce.yildiz.edu.tr](mailto:gokhanb@ce.yildiz.edu.tr)

## Biassing

**Biassing:** The DC voltages applied to a transistor in order to turn it on so that it can amplify the AC signal.
 
## Operating Point

The DC input establishes an operating or *quiescent point* called the **Q-point**.




## The Three States of Operation

- **Active or Linear Region Operation**  
Base-Emitter junction is forward biased  
Base-Collector junction is reverse biased
- **Cutoff Region Operation**  
Base-Emitter junction is reverse biased
- **Saturation Region Operation**  
Base-Emitter junction is forward biased  
Base-Collector junction is forward biased

## DC Biasing Circuits

- Fixed-bias circuit
- Emitter-stabilized bias circuit
- Collector-emitter loop
- Voltage divider bias circuit
- DC bias with voltage feedback

## Fixed Bias

 


## The Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

 


## Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

 

## Saturation

When the transistor is operating in saturation, current through the transistor is at its *maximum* possible value.

$$I_{Csat} = \frac{V_{CC}}{R_C}$$

$$V_{CE} \approx 0 \text{ V}$$

## Load Line Analysis

The end points of the load line are:

$$I_{Csat}$$


$$I_C = V_{CC} / R_C$$

$$V_{CE} = 0 \text{ V}$$

$$V_{CEcutoff}$$

$$V_{CE} = V_{CC}$$


$$I_C = 0 \text{ mA}$$

 

The *Q-point* is the operating point:


- where the value of  $R_B$  sets the value of  $I_B$
- that sets the values of  $V_{CE}$  and  $I_C$

## Circuit Values Affect the Q-Point

 


more ...

## Circuit Values Affect the Q-Point

 


more ...

## Circuit Values Affect the Q-Point

 
 
## Emitter-Stabilized Bias Circuit

Adding a resistor ( $R_E$ ) to the emitter circuit stabilizes the bias circuit.



## Base-Emitter Loop

From Kirchhoff's voltage law:


$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Since  $I_E = (\beta + 1)I_B$ :

$$V_{CC} - I_B R_B - (\beta + 1)I_B R_E = 0$$

Solving for  $I_B$ :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



## Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since  $I_E \cong I_C$ :


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
 
$$V_B = V_{CC} - I_B R_B = V_{BE} + V_E$$




## Improved Biased Stability

Stability refers to a circuit condition in which the currents and voltages will remain fairly constant over a wide range of temperatures and transistor Beta ( $\beta$ ) values.

Adding  $R_E$  to the emitter improves the stability of a transistor.

## Saturation Level

 

The endpoints can be determined from the load line.

$V_{CE\text{cutoff}}$ :

$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$


$I_{C\text{sat}}$ :

$$V_{CE} = 0 \text{ V}$$

$$I_C = \frac{V_{CC}}{R_C + R_E}$$
 
## Voltage Divider Bias

This is a very stable bias circuit.  
The currents and voltages are nearly independent of any variations in  $\beta$ .



## Approximate Analysis

Where  $I_B \ll I_1$  and  $I_1 \cong I_2$ :

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Where  $\beta R_E > 10R_2$ :

$$I_E = \frac{V_E}{R_E}$$


$$V_E = V_B - V_{BE}$$

From Kirchoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 

## Voltage Divider Bias Analysis

Transistor Saturation Level

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:

$$V_{CE} = V_{CC}$$

$$I_C = 0\text{mA}$$


Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE} = 0\text{V}$$
 
## DC Bias with Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.



In this bias circuit the Q-point is only slightly dependent on the transistor beta,  $\beta$ .

## Base-Emitter Loop

From Kirchoff's voltage law:

$$V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Where  $I_B \ll I_C$ :


$$I_C = I_C + I_B \cong I_C$$

Knowing  $I_C = \beta I_B$  and  $I_E \cong I_C$ , the loop equation becomes:

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

Solving for  $I_B$ :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$



## Collector-Emitter Loop

Applying Kirchoff's voltage law:


$$I_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since  $I_C \cong I_C$  and  $I_C = \beta I_B$ :

$$I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

Solving for  $V_{CE}$ :

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 

## Base-Emitter Bias Analysis

### Transistor Saturation Level

$$I_{Csat} = I_{Cmax} = \frac{V_{CC}}{R_C + R_E}$$

### Load Line Analysis

#### Cutoff:

$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$


#### Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE} = 0 \text{ V}$$
 
## Transistor Switching Networks

Transistors with only the DC source applied can be used as electronic switches.



## Switching Circuit Calculations

### Saturation current:

$$I_{Csat} = \frac{V_{CC}}{R_C}$$


### To ensure saturation:

$$I_B > \frac{I_{Csat}}{\beta_{dc}}$$

### Emitter-collector resistance at saturation and cutoff:

$$R_{sat} = \frac{V_{CEsat}}{I_{Csat}}$$

$$R_{cutoff} = \frac{V_{CC}}{I_{CEO}}$$

 


## Switching Time

### Transistor switching times:

$$t_{on} = t_r + t_d$$

$$t_{off} = t_s + t_f$$

 

## Troubleshooting Hints

- Approximate voltages
  - $V_{BE} \cong .7 \text{ V}$  for silicon transistors
  - $V_{CE} \cong 25\% \text{ to } 75\% \text{ of } V_{CC}$
- Test for opens and shorts with an ohmmeter.
- Test the solder joints.
- Test the transistor with a transistor tester or a curve tracer.
- Note that the load or the next stage affects the transistor operation.

## PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.