

Electronic Circuits

Prof. Nizamettin AYDIN

naydin@yildiz.edu.tr

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

gokhanb@ce.yildiz.edu.tr

1

FET Amplifiers

FETs provide:

- Excellent voltage gain
- High input impedance
- Low-power consumption
- Good frequency range

2

FET Small-Signal Model

Transconductance


The relationship of a change in I_D to the corresponding change in V_{GS} is called **transconductance**

Transconductance is denoted g_m and given by:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

3

Graphical Determination of g_m

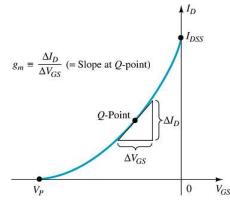

4

Mathematical Definitions of g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$\text{Where } V_{GS} = 0V \quad g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$\text{Where } 1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_D}{I_{DSS}}}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

5

FET Impedance

Input impedance:

$$Z_i = \infty \Omega$$

Output Impedance:

$$Z_o = r_d = \frac{1}{y_{os}}$$


where:

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS} = \text{constant}}$$

y_{os} = admittance parameter listed on FET specification sheets.

6

FET AC Equivalent Circuit

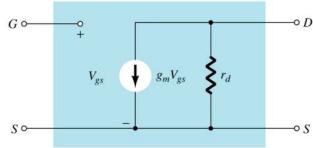


7

Common-Source (CS) Fixed-Bias Circuit

The input is on the gate and the output is on the drain

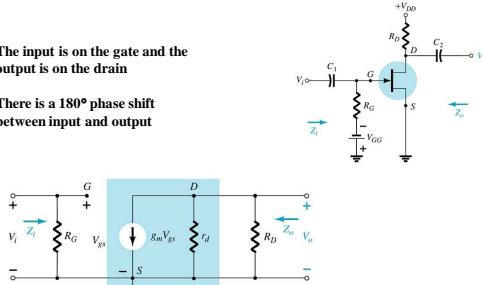There is a 180° phase shift between input and output



8

Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:

$$Z_o = R_D \parallel r_d$$

$$Z_o \approx R_D \quad | \quad r_d \geq 10R_D$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -g_m(r_d \parallel R_D)$$


$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad | \quad r_d \geq 10R_D$$

9

Common-Source (CS) Self-Bias Circuit

This is a common-source amplifier configuration, so the input is on the gate and the output is on the drain

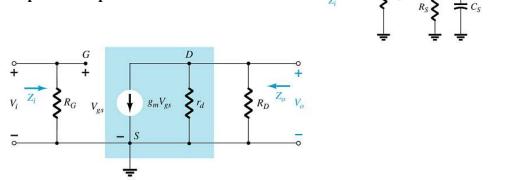There is a 180° phase shift between input and output



10

Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:

$$Z_o = r_d \parallel R_D$$

$$Z_o \approx R_D \quad | \quad r_d \geq 10R_D$$

Voltage gain:


$$A_v = -g_m(r_d \parallel R_D)$$

$$A_v = -g_m R_D \quad | \quad r_d \geq 10R_D$$







11

Common-Source (CS) Self-Bias Circuit

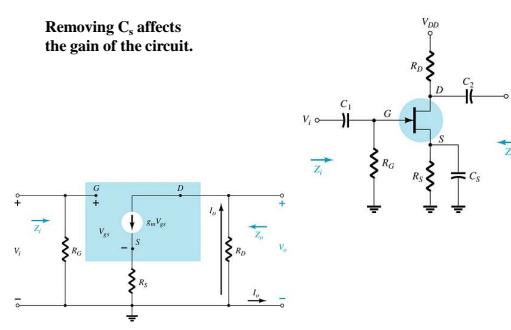Removing C_s affects the gain of the circuit.



12

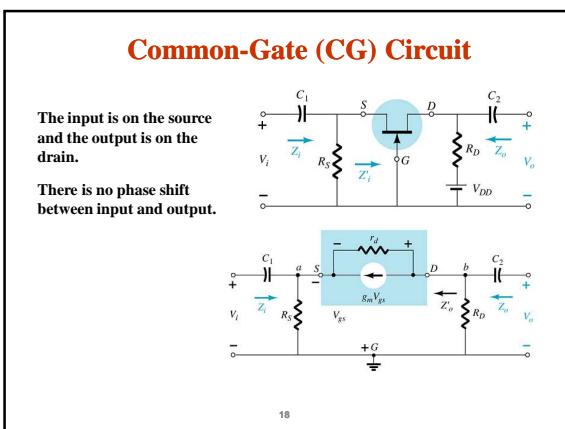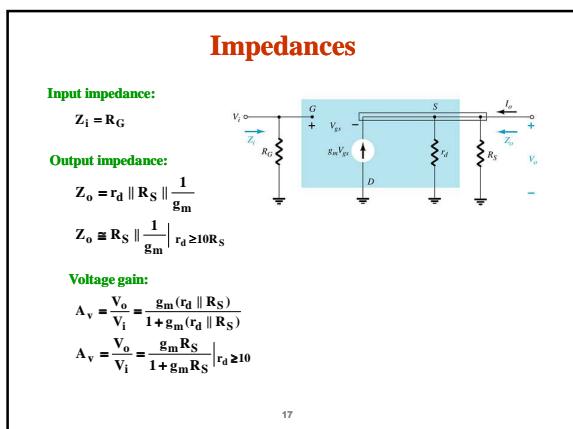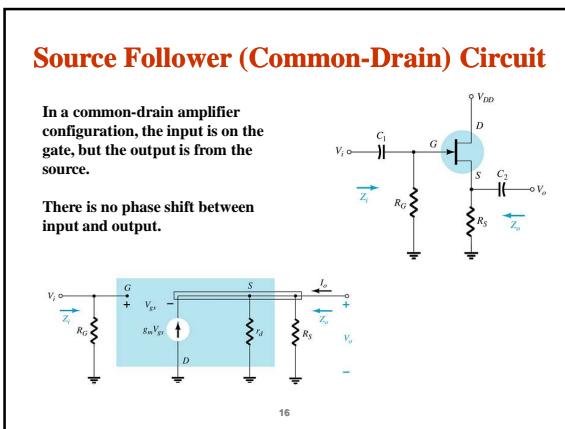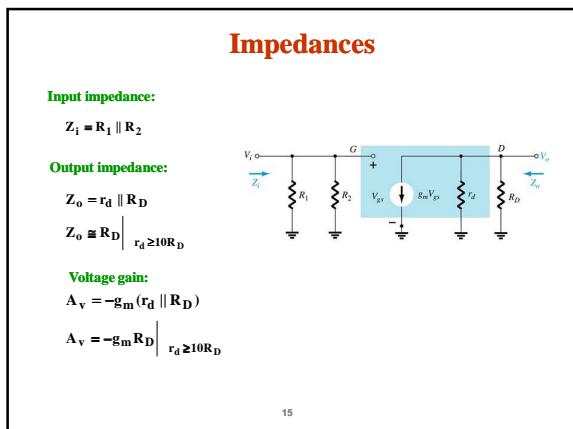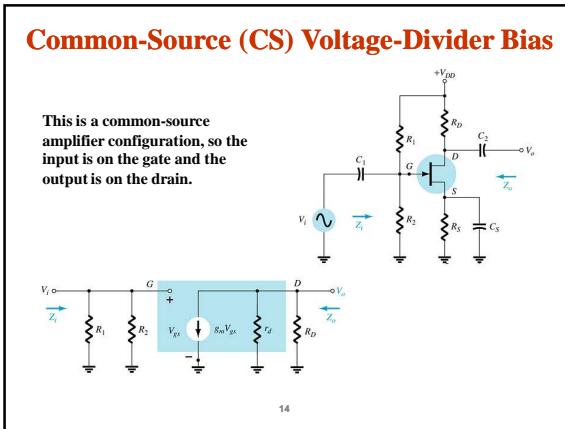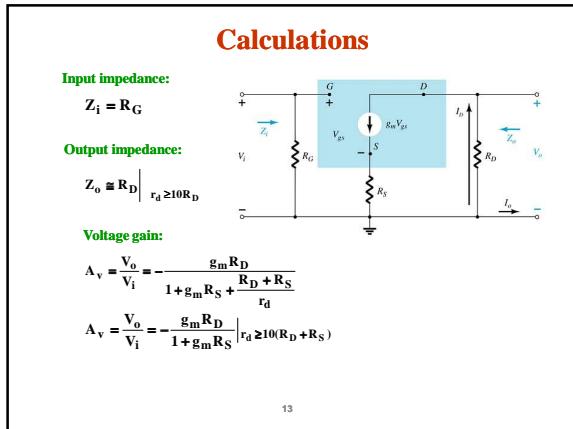

Calculations

Input impedance:

$$Z_i = R_1 \parallel R_2$$

Output impedance:


$$Z_o = r_d \parallel R_D$$

$$Z_o \approx R_D \mid r_d \geq 10R_D$$

Voltage gain:


$$A_v = -g_m (r_d \parallel R_D)$$
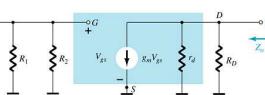
$$A_v \approx -g_m R_D \mid r_d \geq 10R_D$$



25


Summary Table

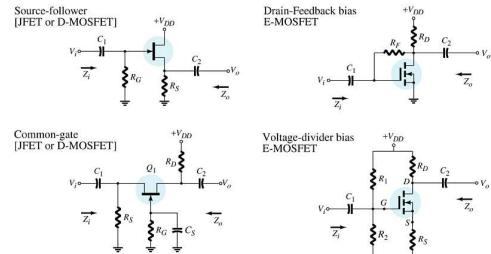

more...

26

Summary Table

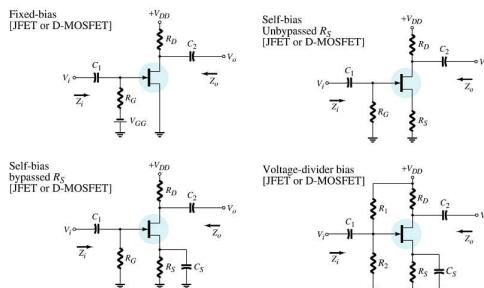

27

Troubleshooting

Check the DC bias voltages:

If not correct check power supply, resistors, FET. Also check to ensure that the coupling capacitor between amplifier stages is OK.

Check the AC voltages:

If not correct check FET, capacitors and the loading effect of the next stage

28

Practical Applications

Three-Channel Audio Mixer
Silent Switching
Phase Shift Networks
Motion Detection System

29