

Electronic Circuits Elektronik Devreler


Prof. Dr. Nizamettin AYDIN

naydin@yildiz.edu.tr

<http://www.yildiz.edu.tr/~naydin>

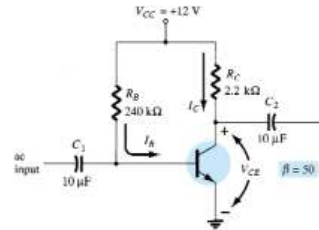Example 1

- Determine the following for the fixed-bias configuration shown in the figure.



- (a) I_{BQ} and I_{CQ}
- (b) V_{CEQ}
- (c) V_B and V_C
- (d) V_{BC}
- (e) Determine the saturation current I_{Csat}

Solution

$$(a) \quad I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \text{ }\mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \text{ }\mu\text{A}) = 2.35 \text{ mA}$$

$$(b) \quad V_{CEQ} = V_{CC} - I_{CQ}R_C \\ = 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ = 6.83 \text{ V}$$

$$(c) \quad V_B = V_{BE} = 0.7 \text{ V} \\ V_C = V_{CE} = 6.83 \text{ V}$$

(d) Using double-subscript notation yields


$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V} \\ = -6.13 \text{ V}$$

with the negative sign revealing that the junction is reversed-biased, as it should be for linear amplification.

$$(e) \quad I_{Csat} = \frac{V_{CC}}{R_C} = \frac{12 \text{ V}}{2.2 \text{ k}\Omega} = 5.45 \text{ mA}$$

Example 2

- Given the following load line and the defined Q-point, determine the required values of V_{CC} , R_C , and R_B for a fixed-bias configuration.

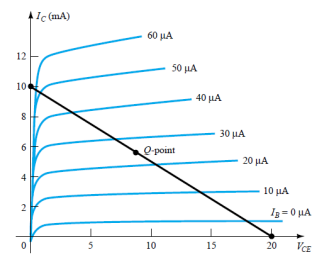

Solution 2

- From the figure

$$V_{CE} = V_{CC} = 20 \text{ V at } I_C = 0 \text{ mA}$$

$$I_C = \frac{V_{CC}}{R_C} \text{ at } V_{CE} = 0 \text{ V}$$


$$R_C = \frac{V_{CC}}{I_C} = \frac{20 \text{ V}}{10 \text{ mA}} = 2 \text{ k}\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20 \text{ V} - 0.7 \text{ V}}{25 \text{ }\mu\text{A}} = 772 \text{ k}\Omega$$

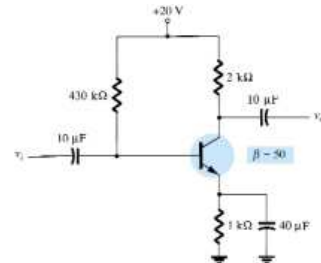Example 3

- For the following emitter bias network, determine:



- (a) I_B
- (b) I_C
- (c) V_{CE}
- (d) V_C
- (e) V_E
- (f) V_B
- (g) V_{BC}

Solution 3...

(a)
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)}$$

$$= \frac{19.3 \text{ V}}{481 \text{ k}\Omega} = 40.1 \mu\text{A}$$

(b)
$$I_C = \beta I_B$$

$$= (50)(40.1 \mu\text{A})$$

$$\approx 2.01 \text{ mA}$$

(c)
$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 20 \text{ V} - 6.03 \text{ V}$$

$$= 13.97 \text{ V}$$

(d)
$$V_C = V_{CC} - I_C R_C$$

$$= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega) = 20 \text{ V} - 4.02 \text{ V}$$

$$= 15.98 \text{ V}$$

7

...Solution 3

(e)
$$V_E = V_C - V_{CE}$$

$$= 15.98 \text{ V} - 13.97 \text{ V}$$

$$= 2.01 \text{ V}$$

or
$$V_E = I_E R_E \approx I_C R_E$$

$$= (2.01 \text{ mA})(1 \text{ k}\Omega)$$

$$= 2.01 \text{ V}$$

(f)
$$V_B = V_{BE} + V_E$$

$$= 0.7 \text{ V} + 2.01 \text{ V}$$

$$= 2.71 \text{ V}$$

(g)
$$V_{BC} = V_B - V_C$$

$$= 2.71 \text{ V} - 15.98 \text{ V}$$

$$= -13.27 \text{ V} \quad (\text{reverse-biased as required})$$

8


Example 4

- Determine the saturation current for the network of Example 3.
- Solution:

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$$

$$= \frac{20 \text{ V}}{2 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{20 \text{ V}}{3 \text{ k}\Omega}$$


$$= 6.67 \text{ mA}$$

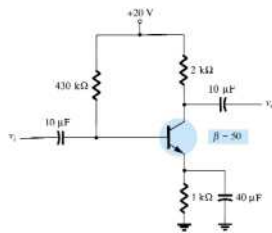

9

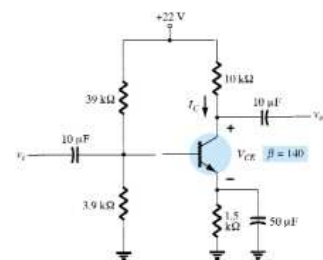Example 5

- Determine the dc bias voltage V_{CE} and the current I_C for the following voltage-divider network configuration.



10

Solution 5

$$R_{Th} = R_1 || R_2 = \frac{(39 \text{ k}\Omega)(3.9 \text{ k}\Omega)}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 3.55 \text{ k}\Omega$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(3.9 \text{ k}\Omega)(22 \text{ V})}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 2 \text{ V}$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E} = \frac{2 \text{ V} - 0.7 \text{ V}}{3.55 \text{ k}\Omega + (141)(1.5 \text{ k}\Omega)} = \frac{1.3 \text{ V}}{3.55 \text{ k}\Omega + 211.5 \text{ k}\Omega}$$

$$= 6.05 \mu\text{A}$$


$$I_C = \beta I_B = (140)(6.05 \mu\text{A}) = 0.85 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E) = 22 \text{ V} - (0.85 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega) = 22 \text{ V} - 9.78 \text{ V} = 12.22 \text{ V}$$

11

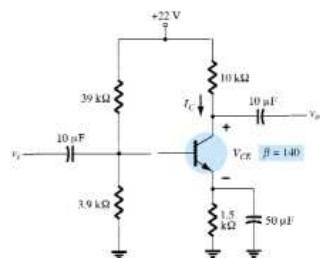Example 6

- Repeat the exact analysis of Example 5 if β is reduced to 70, and compare solutions for I_{CQ} and V_{CEQ} .



12

Solution 6

$$R_{Th} = 3.55 \text{ k}\Omega, \quad E_{Th} = 2 \text{ V}$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$= \frac{2 \text{ V} - 0.7 \text{ V}}{3.55 \text{ k}\Omega + (71)(1.5 \text{ k}\Omega)} = \frac{1.3 \text{ V}}{3.55 \text{ k}\Omega + 106.5 \text{ k}\Omega}$$

$$= 11.81 \text{ }\mu\text{A}$$

$$I_{C_Q} = \beta I_B$$

$$= (70)(11.81 \text{ }\mu\text{A})$$

$$= 0.83 \text{ mA}$$

$$V_{CE_Q} = V_{CC} - I_C(R_C + R_E)$$

$$= 22 \text{ V} - (0.83 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega)$$

$$= 12.46 \text{ V}$$


- The results clearly show the relative insensitivity of the circuit to the change in β .
- Even though β is drastically cut in half, from 140 to 70, the levels of I_{C_Q} and V_{CE_Q} are essentially the same

β	I_{C_Q} (mA)	V_{CE_Q} (V)
140	0.85	12.22
70	0.83	12.46

13

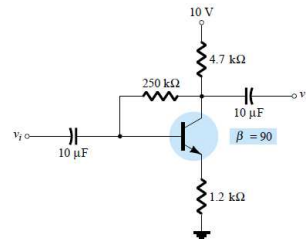Example 7

- Determine the quiescent levels of I_{C_Q} and V_{CE_Q} for the following network.



14

Solution 7

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

$$= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)}$$

$$= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega}$$

$$= 11.91 \text{ }\mu\text{A}$$

$$I_{C_Q} = \beta I_B = (90)(11.91 \text{ }\mu\text{A})$$

$$= 1.07 \text{ mA}$$

$$V_{CE_Q} = V_{CC} - I_C(R_C + R_E)$$

$$= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)$$

$$= 10 \text{ V} - 6.31 \text{ V}$$


$$= 3.69 \text{ V}$$

15

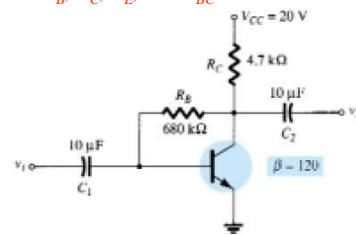Example 8

- For the following network:

- Determine I_{C_Q} and V_{CE_Q}
- Find V_B , V_C , V_E , and V_{BC} .



16

Solution 8

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$

$$= \frac{20 \text{ V} - 0.7 \text{ V}}{680 \text{ k}\Omega + (120)(4.7 \text{ k}\Omega)} = \frac{19.3 \text{ V}}{1.244 \text{ M}\Omega}$$

$$= 15.51 \text{ }\mu\text{A}$$

$$I_{C_Q} = \beta I_B = (120)(15.51 \text{ }\mu\text{A})$$

$$= 1.86 \text{ mA}$$

$$V_{CE_Q} = V_{CC} - I_C R_C$$

$$= 20 \text{ V} - (1.86 \text{ mA})(4.7 \text{ k}\Omega)$$

$$= 11.26 \text{ V}$$

$$V_B = V_{BE} = 0.7 \text{ V}$$

$$V_C = V_{CE} = 11.26 \text{ V}$$

$$V_E = 0 \text{ V}$$


$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 11.26 \text{ V}$$

$$= -10.56 \text{ V}$$

17

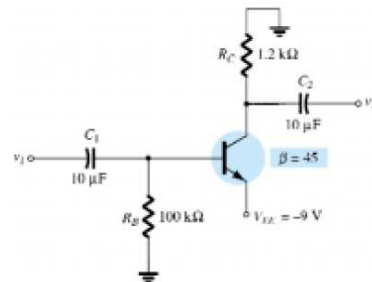Example 9

- Determine V_C and V_B for the following network.



18

Solution 9


$$\begin{aligned}
 -I_B R_B - V_{BE} + V_{EE} &= 0 & I_C &= \beta I_B \\
 I_B &= \frac{V_{EE} - V_{BE}}{R_B} & &= (45)(83 \mu\text{A}) \\
 & & &= 3.735 \text{ mA} \\
 I_B &= \frac{9 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} & V_C &= -I_C R_C \\
 & & &= -(3.735 \text{ mA})(1.2 \text{ k}\Omega) \\
 & & &= -4.48 \text{ V} \\
 & & V_B &= -I_B R_B \\
 & & &= -(83 \mu\text{A})(100 \text{ k}\Omega) \\
 & & &= -8.3 \text{ V}
 \end{aligned}$$

19

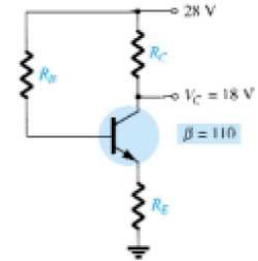Example 10

The following emitter-bias configuration has the following specifications:

$$\begin{aligned}
 I_{CQ} &= \frac{1}{2} I_{C\text{sat}}, \\
 I_{C\text{sat}} &= 8 \text{ mA}, \\
 V_{CC} &= 28 \text{ V} \\
 V_C &= 18 \text{ V}, \text{ and} \\
 \beta &= 110.
 \end{aligned}$$



Determine R_C , R_E , and R_B .

20


Solution 10

$$\begin{aligned}
 I_{CQ} &= \frac{1}{2} I_{C\text{sat}} = 4 \text{ mA} & I_{BQ} &= \frac{I_{CQ}}{\beta} = \frac{4 \text{ mA}}{110} = 36.36 \mu\text{A} \\
 R_C &= \frac{V_{R_C}}{I_{CQ}} = \frac{V_{CC} - V_C}{I_{CQ}} & I_{BQ} &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \\
 &= \frac{28 \text{ V} - 18 \text{ V}}{4 \text{ mA}} = 2.5 \text{ k}\Omega & R_B + (\beta + 1)R_E &= \frac{V_{CC} - V_{BE}}{I_{BQ}} \\
 I_{C\text{sat}} &= \frac{V_{CC}}{R_C + R_E} & R_B &= \frac{V_{CC} - V_{BE}}{I_{BQ}} - (\beta + 1)R_E \\
 R_C + R_E &= \frac{V_{CC}}{I_{C\text{sat}}} = \frac{28 \text{ V}}{8 \text{ mA}} = 3.5 \text{ k}\Omega & &= \frac{28 \text{ V} - 0.7 \text{ V}}{36.36 \mu\text{A}} - (111)(1 \text{ k}\Omega) \\
 R_E &= 3.5 \text{ k}\Omega - R_C & &= \frac{27.3 \text{ V}}{36.36 \mu\text{A}} - 111 \text{ k}\Omega \\
 &= 3.5 \text{ k}\Omega - 2.5 \text{ k}\Omega & &= 639.8 \text{ k}\Omega \\
 &= 1 \text{ k}\Omega & &
 \end{aligned}$$

21

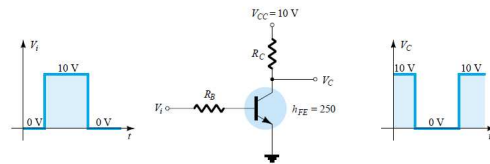Example 11

- Determine R_B and R_C for the following transistor inverter if $I_{C\text{sat}} = 10 \text{ mA}$.



22

Solution 11...

At saturation:

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$

and

$$10 \text{ mA} = \frac{10 \text{ V}}{R_C}$$

so that

$$R_C = \frac{10 \text{ V}}{10 \text{ mA}} = 1 \text{ k}\Omega$$

At saturation:

$$I_B = \frac{I_{C\text{sat}}}{\beta_{\text{dc}}} = \frac{10 \text{ mA}}{250} = 40 \mu\text{A}$$

Choosing $I_B = 60 \mu\text{A}$ to ensure saturation and using

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B}$$

23

...Solution 11

we obtain
$$R_B = \frac{V_i - 0.7 \text{ V}}{I_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{60 \mu\text{A}} = 155 \text{ k}\Omega$$

Choose $R_B = 150 \text{ k}\Omega$, which is a standard value. Then

$$I_B = \frac{V_i - 0.7 \text{ V}}{R_B} = \frac{10 \text{ V} - 0.7 \text{ V}}{150 \text{ k}\Omega} = 62 \mu\text{A}$$

and


$$I_B = 62 \mu\text{A} > \frac{I_{C\text{sat}}}{\beta_{\text{dc}}} = 40 \mu\text{A}$$

Therefore, use $R_B = 150 \text{ k}\Omega$ and $R_C = 1 \text{ k}\Omega$.

24

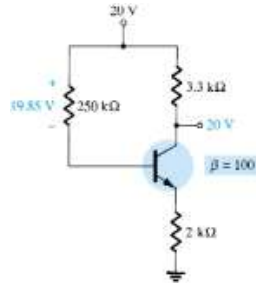Example 12

- Based on the readings provided in the following network, determine whether the network is operating properly and, if not, the probable cause.



25

Solution 12

The 20 V at the collector immediately reveals that $I_C = 0$ mA, due to an open circuit or a nonoperating transistor. The level of $V_{R_B} = 19.85$ V also reveals that the transistor is "off" since the difference of $V_{CC} - V_{R_B} = 0.15$ V is less than that required to turn "on" the transistor and provide some voltage for V_E . In fact, if we assume a short circuit condition from base to emitter, we obtain the following current through R_B :

$$I_{R_B} = \frac{V_{CC}}{R_B + R_E} = \frac{20 \text{ V}}{252 \text{ k}\Omega} = 79.4 \mu\text{A}$$

which matches that obtained from

$$I_{R_B} = \frac{V_{R_B}}{R_B} = \frac{19.85 \text{ V}}{250 \text{ k}\Omega} = 79.4 \mu\text{A}$$

If the network were operating properly, the base current should be


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (101)(2 \text{ k}\Omega)} = \frac{19.3 \text{ V}}{452 \text{ k}\Omega} = 42.7 \mu\text{A}$$

The result, therefore, is that the transistor is in a damaged state, with a short-circuit condition between base and emitter.

26

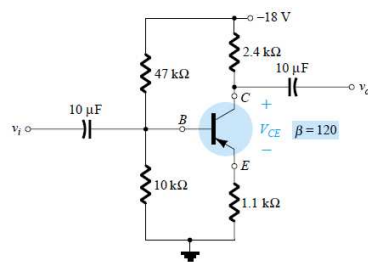Example 13

- Determine V_{CE} for the following voltage-divider bias configuration.



27

Solution 13...

Testing the condition

$$\beta R_E \geq 10R_2$$

results in

$$(120)(1.1 \text{ k}\Omega) \geq 10(10 \text{ k}\Omega)$$

$$132 \text{ k}\Omega \geq 100 \text{ k}\Omega \text{ (satisfied)}$$

Solving for V_B , we have

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(10 \text{ k}\Omega)(-18 \text{ V})}{47 \text{ k}\Omega + 10 \text{ k}\Omega} = -3.16 \text{ V}$$

Note the similarity in format of the equation with the resulting negative voltage for V_B .

Applying Kirchhoff's voltage law around the base-emitter loop yields

$$+V_B - V_{BE} - V_E = 0$$

and

$$V_E = V_B - V_{BE}$$

Substituting values, we obtain

$$\begin{aligned} V_E &= -3.16 \text{ V} - (-0.7 \text{ V}) \\ &= -3.16 \text{ V} + 0.7 \text{ V} \\ &= -2.46 \text{ V} \end{aligned}$$

28

...Solution 13

Note in the equation above that the standard single- and double-subscript notation is employed. For an *npn* transistor the equation $V_E = V_B - V_{BE}$ would be exactly the same. The only difference surfaces when the values are substituted.

The current

$$I_E = \frac{V_E}{R_E} = \frac{2.46 \text{ V}}{1.1 \text{ k}\Omega} = 2.24 \text{ mA}$$

For the collector-emitter loop:

$$-I_E R_E + V_{CE} - I_C R_C + V_{CC} = 0$$

Substituting $I_E \approx I_C$ and gathering terms, we have

$$V_{CE} = -V_{CC} + I_C(R_C + R_E)$$

Substituting values gives

$$\begin{aligned} V_{CE} &= -18 \text{ V} + (2.24 \text{ mA})(2.4 \text{ k}\Omega + 1.1 \text{ k}\Omega) \\ &= -18 \text{ V} + 7.84 \text{ V} \\ &= -10.16 \text{ V} \end{aligned}$$

29