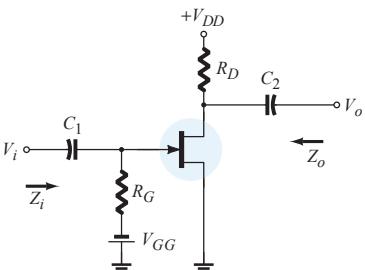
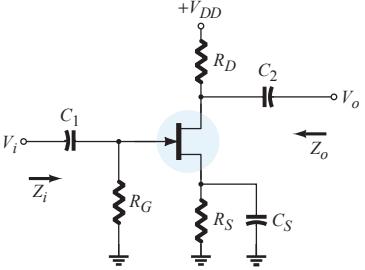
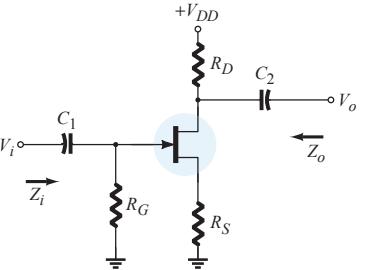
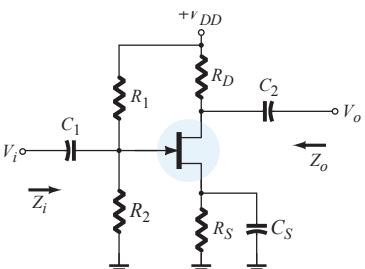
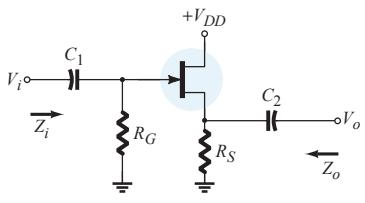
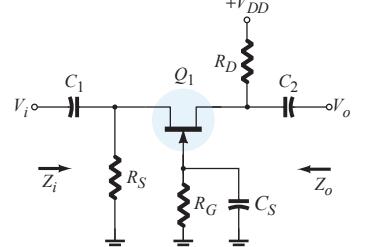
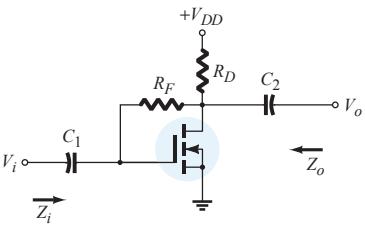
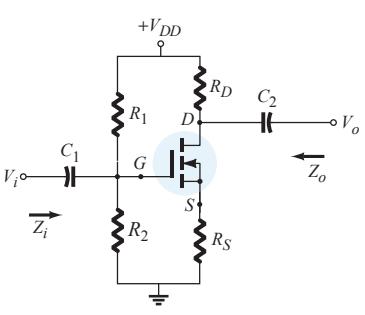


**TABLE 9.1** Z<sub>i</sub>, Z<sub>o</sub>, and A<sub>v</sub> for various FET configurations

Configuration	Z <sub>i</sub>	Z <sub>o</sub>	A <sub>v</sub> = V <sub>o</sub> / V <sub>i</sub>
Fixed-bias [JFET or D-MOSFET]	 <p>High (10 MΩ)  <math>= [R_G]</math></p>	<p>Medium (2 kΩ)</p> $= [R_D \  r_d]$ $\cong [R_D] \quad (r_d \geq 10 R_D)$	<p>Medium (-10)</p> $= [-g_m(r_d \  R_D)]$ $\cong [-g_m R_D] \quad (r_d \geq 10 R_D)$
Self-bias bypassed R <sub>s</sub> [JFET or D-MOSFET]	 <p>High (10 MΩ)  <math>= [R_G]</math></p>	<p>Medium (2 kΩ)</p> $= [R_D \  r_d]$ $\cong [R_D] \quad (r_d \geq 10 R_D)$	<p>Medium (-10)</p> $= [-g_m(r_d \  R_D)]$ $\cong [-g_m R_D] \quad (r_d \geq 10 R_D)$
Self-bias unbypassed R <sub>s</sub> [JFET or D-MOSFET]	 <p>High (10 MΩ)  <math>= [R_G]</math></p>	$= \frac{\left[ 1 + g_m R_s + \frac{R_s}{r_d} \right] R_d}{\left[ 1 + g_m R_s + \frac{R_s}{r_d} + \frac{R_d}{r_d} \right]}$ $= [R_D] \quad r_d \geq 10 R_D \text{ or } r_d = \infty \Omega$	<p>Low (-2)</p> $= \frac{g_m R_D}{1 + g_m R_s + \frac{R_D + R_s}{r_d}}$ $\cong -\frac{g_m R_D}{1 + g_m R_s} \quad [r_d \geq 10(R_d + R_s)]$
Voltage-divider bias [JFET or D-MOSFET]	 <p>High (10 MΩ)  <math>= [R_1 \  R_2]</math></p>	<p>Medium (2 kΩ)</p> $= [R_D \  r]$ $\cong [R_D] \quad (r_d \geq 10 R_D)$	<p>Medium (-10)</p> $= [-g_m(r_d \  R_D)]$ $\cong [-g_m R_D] \quad (r_d \geq 10 R_D)$

$g_m$

TABLE 9.1 (Continued)

Configuration	$Z_i$	$Z_o$	$A_v = \frac{V_o}{V_i}$
Source-follower [JFET or D-MOSFET]	 <p>High (<math>10 \text{ M}\Omega</math>)  <math>= [R_G]</math></p>	<p>Low (<math>100 \text{ k}\Omega</math>)  <math>= [r_d \  R_S \  1/g_m]</math>  <math>\cong [R_S \  1/g_m] \quad (r_d \geq 10 R_S)</math></p>	<p>Low (<math>&lt; 1</math>)  <math>= \frac{g_m(r_d \  R_S)}{1 + g_m(r_d \  R_S)}</math>  <math>\cong \frac{g_m R_S}{1 + g_m R_S} \quad (r_d \geq 10 R_S)</math></p>
Common-gate [JFET or D-MOSFET]	 <p>Low (<math>1 \text{ k}\Omega</math>)  <math>= [R_S \  \frac{r_d + R_D}{1 + g_m r_d}]</math>  <math>\cong [R_S \  \frac{1}{g_m}] \quad (r_d \geq 10 R_D)</math></p>	<p>Medium (<math>2 \text{ k}\Omega</math>)  <math>= [R_D \  r_d]</math>  <math>\cong [R_D] \quad (r_d \geq 10 R_D)</math></p>	<p>Medium (+10)  <math>= \frac{g_m R_D + \frac{R_D}{r_d}}{1 + \frac{R_D}{r_d}}</math>  <math>\cong [g_m R_D] \quad (r_d \geq 10 R_S)</math></p>
Drain-feedback bias E-MOSFET	 <p>Medium (<math>1 \text{ M}\Omega</math>)  <math>= \frac{R_F + r_d \  R_D}{1 + g_m(r_d \  R_D)}</math>  <math>\cong \frac{R_F}{1 + g_m R_D} \quad (r_d \geq 10 R_D)</math></p>	<p>Medium (<math>2 \text{ k}\Omega</math>)  <math>= [R_F \  r_d \  R_D]</math>  <math>\cong [R_D] \quad (R_F, r_d \geq 10 R_D)</math></p>	<p>Medium (-10)  <math>= -g_m(R_F \  r_d \  R_D)</math>  <math>\cong -g_m R_D \quad (R_F, r_d \geq 10 R_D)</math></p>
Voltage-divider bias E-MOSFET	 <p>Medium (<math>1 \text{ M}\Omega</math>)  <math>= [R_1 \  R_2]</math></p>	<p>Medium (<math>2 \text{ k}\Omega</math>)  <math>= [R_D \  r_d]</math>  <math>\cong [R_D] \quad (R_d \geq 10 R_D)</math></p>	<p>Medium (-10)  <math>= -g_m(r_d \  R_D)</math>  <math>\cong -g_m R_D \quad (r_d \geq 10 R_D)</math></p>