

Introduction to Digital Logic

Prof. Nizamettin AYDIN

naydin@yildiz.edu.tr

naydin@ieee.org

1

Course Outline

1. Digital Computers, Number Systems, Arithmetic Operations, Decimal, Alphanumeric, and Gray Codes
2. Binary Logic, Gates, Boolean Algebra, Standard Forms
3. Circuit Optimization, Two-Level Optimization, Map Manipulation, Multi-Level Circuit Optimization
4. **Additional Gates and Circuits, Other Gate Types, Exclusive-OR Operator and Gates, High-Impedance Outputs**
5. Implementation Technology and Logic Design, Design Concepts and Automation, The Design Space, Design Procedure, The major design steps
6. Programmable Implementation Technologies: Read-Only Memories, Programmable Logic Arrays, Programmable Array Logic, Technology mapping to programmable logic devices
7. Combinational Functions and Circuits
8. Arithmetic Functions and Circuits
9. Sequential Circuits Storage Elements and Sequential Circuit Analysis
10. Sequential Circuits, Sequential Circuit Design State Diagrams, State Tables
11. Counters, register cells, buses, & serial operations
12. Sequencing and Control, Datapath and Control, Algorithmic State Machines (ASM)
13. Memory Basics

2

Introduction to Digital Logic

Lecture 4

Additional Gates and Circuits

- Other Gate Types
- Exclusive-OR Operator and Gates
- High-Impedance Outputs

3

Other Gate Types

- Why?
 - Implementation feasibility and low cost
 - Power in implementing Boolean functions
 - Convenient conceptual representation
- Gate classifications
 - Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).
 - Complex gate - a gate that requires more than one primitive operation type for its description
- Primitive gates will be covered first

4

Buffer

- A buffer is a gate with the function $F = X$:




- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.

5

NAND Gate

- The basic NAND gate has the following symbol, illustrated for three inputs:

– AND-Invert (NAND)

 


- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle ("bubble") represents the invert function.

6

NAND Gates (continued)

 - Applying DeMorgan's Law gives Invert-OR (NAND)



- This NAND symbol is called Invert-OR, since inputs are inverted and then ORed together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.

7

NAND Gates (continued)


- The NAND gate is the natural implementation for the simplest and fastest electronic circuits
- Universal gate* - a gate type that can implement any Boolean function.
- The NAND gate is a universal gate
- NAND usually does not have an operation symbol defined since
 - the NAND operation is not associative, and
 - we have difficulty dealing with non-associative mathematics!

8

NOR Gate

- The basic NOR gate has the following symbol, illustrated for three inputs:

– OR-Invert (NOR)

 


- NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert. The small circle ("bubble") represents the invert function.

9

NOR Gate (continued)

 - Applying DeMorgan's Law gives Invert-AND (NOR)



- This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.

10

NOR Gate (continued)

- The NOR gate is another natural implementation for the simplest and fastest electronic circuits
- The NOR gate is a universal gate
- NOR usually does not have a defined operation symbol since
 - the NOR operation is not associative, and
 - we have difficulty dealing with non-associative mathematics!

11

Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The XOR function may be;
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

12

Exclusive OR/ Exclusive NOR

- Uses for the XOR and XNORs gate include:
 - Adders/subtractors/multipliers
 - Counters/incrementers/decrementers
 - Parity generators/checkers
- Definitions
 - The XOR function is: $X \oplus Y = X\bar{Y} + \bar{X}Y$
 - The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is: $\bar{X} \oplus \bar{Y} = XY + \bar{X}\bar{Y}$
- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

13

Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$(X \oplus Y)$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:
X OR Y, but NOT BOTH
- Why is the XNOR function also known as the *equivalence* function, denoted by the operator \equiv ?

14

XOR/XNOR (Continued)

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$X \oplus Y \oplus Z = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

- The complement of the odd function is the even function.
- The XOR identities:

$$\begin{aligned} X \oplus 0 &= X & X \oplus 1 &= \bar{X} \\ X \oplus X &= 0 & X \oplus \bar{X} &= 1 \\ X \oplus Y &= Y \oplus X \\ (X \oplus Y) \oplus Z &= X \oplus (Y \oplus Z) = X \oplus Y \oplus Z \end{aligned}$$


15

Symbols For XOR and XNOR

- XOR symbol:



- XNOR symbol:

 


- Symbols exist only for two inputs


16

XOR Implementations

 - The simple SOP implementation uses the following structure:



- A NAND only implementation is:

 

17


Odd and Even Functions

- The odd and even functions on a K-map form "checkerboard" patterns.
- The 1s of an odd function correspond to minterms having an index with an odd number of 1s.
- The 1s of an even function correspond to minterms having an index with an even number of 1s.
- Implementation of odd and even functions for greater than 4 variables as a two-level circuit is difficult, so we use "trees" made up of :
 - 2-input XOR or XNORs
 - 3- or 4-input odd or even functions

18

 Example: Odd Function Implementation


- Design a 3-input odd function $F = X \oplus Y \oplus Z$ with 2-input XOR gates
- Factoring, $F = (X \oplus Y) \oplus Z$
- The circuit:



19

 Example: Even Function Implementation


- Design a 4-input odd function $F = W \oplus X \oplus Y \oplus Z$ with 2-input XOR and XNOR gates
- Factoring, $F = (W \oplus X) \oplus (Y \oplus Z)$
- At the second level use XNOR instead of XOR:



20

Parity Generators and Checkers

- In Chapter 1, a parity bit added to n-bit code to produce an n + 1 bit code:
 - Add odd parity bit to generate code words with even parity
 - Add even parity bit to generate code words with odd parity
 - Use odd parity circuit to check code words with even parity
 - Use even parity circuit to check code words with odd parity
- Example: n = 3. Generate even parity code words of length 4 with odd parity generator:
 - Check even parity code words of length 4 with odd parity checker:
- Operation: (X,Y,Z) = (0,0,1) gives (X,Y,Z,P) = (0,0,1,1) and E = 0. If Y changes from 0 to 1 between generator and checker, then E = 1 indicates an error.

 

21

Hi-Impedance Outputs

- Logic gates introduced thus far
 - have 1 and 0 output values,
 - cannot have their outputs connected together, and
 - transmit signals on connections in only one direction.
- Three-state logic adds a third logic value, Hi-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.
- The presence of a Hi-Z state makes a gate output as described above behave quite differently:
 - "1 and 0" become "1, 0, and Hi-Z"
 - "cannot" becomes "can," and
 - "only one" becomes "two"

22


Hi-Impedance Outputs (continued)

- What is a Hi-Z value?
 - The Hi-Z value behaves as an open circuit
 - This means that, looking back into the circuit, the output appears to be disconnected.
 - It is as if a switch between the internal circuitry and the output has been opened.
- Hi-Z may appear on the output of any gate, but we restrict gates to:
 - a 3-state buffer, or
 - a transmission gate,
 each of which has one data input and one control input.

23

The 3-State Buffer

 - For the symbol and truth table, IN is the data input, and EN, the control input.
- For EN = 0, regardless of the value on IN (denoted by X), the output value is Hi-Z.
- For EN = 1, the output value follows the input value.
- Variations:
 - Data input, IN, can be inverted
 - Control input, EN, can be inverted by addition of "bubbles" to signals.



24

Resolving 3-State Values on a Connection

- Connection of two 3-state buffer outputs, B1 and B0, to a wire, OUT
- Assumption: Buffer data inputs can take on any combination of values 0 and 1
- Resulting Rule: At least one buffer output value must be Hi-Z. Why?
- How many valid buffer output combinations exist?
- What is the rule for n 3-state buffers connected to wire, OUT?
- How many valid buffer output combinations exist?


Resolution Table		
B1	B0	OUT
0	Hi-Z	0
1	Hi-Z	1
Hi-Z	0	0
Hi-Z	1	1
Hi-Z	Hi-Z	Hi-Z

25

3-State Logic Circuit

- Data Selection Function: If $s = 0$, $OL = IN0$, else $OL = IN1$
- Performing data selection with 3-state buffers:

EN0	IN0	EN1	IN1	OL
0	X	1	0	0
0	X	1	1	1
1	0	0	X	0
1	1	0	X	1
0	X	0	X	X

 


- Since $EN0 = \bar{S}$ and $EN1 = S$, one of the two buffer outputs is always Hi-Z plus the last row of the table never occurs.

26

Transmission Gates

 - The transmission gate is one of the designs for an electronic switch for connecting and disconnecting two points in a circuit:



27


Transmission Gates (continued)

- In many cases, X can be regarded as a data input and Y as an output. C and \bar{C} , with complementary values applied, is a control input.
- With these definitions, the transmission gate, provides a 3-state output:
 - $C = 1$, $Y = X$ ($X = 0$ or 1)
 - $C = 0$, $Y = \text{Hi-Z}$
- Care must be taken when using the TG in design, however, since X and Y as input and output are interchangeable, and signals can pass in both directions.

28

Circuit Example Using TG

- Exclusive OR $F = A \oplus C$

 

- The basis for the function implementation is TG-controlled paths to the output

29

More Complex Gates

- The remaining complex gates are SOP or POS structures with and without an output inverter.
- The names are derived using:
 - A - AND
 - O - OR
 - I - Inverter
 - Numbers of inputs on first-level "gates" or directly to second-level "gates"

30

More Complex Gates (continued)

- Example: AOI - AND-OR-Invert consists of a single gate with AND functions driving an OR function which is inverted.
- Example: 2-2-1 AO has two 2-input ANDS driving an OR with one additional OR input
- These gate types are used because:
 - the number of transistors needed is fewer than required by connecting together primitive gates
 - potentially, the circuit delay is smaller, increasing the circuit operating speed

31