

Introduction to Digital Logic

Prof. Nizamettin AYDIN

naydin@yildiz.edu.tr

naydin@ieee.org

1

Course Outline

1. Digital Computers, Number Systems, Arithmetic Operations, Decimal, Alphanumeric, and Gray Codes
2. Binary Logic, Gates, Boolean Algebra, Standard Forms
3. Circuit Optimization, Two-Level Optimization, Map Manipulation, Multi-Level Circuit Optimization
4. Additional Gates and Circuits, Other Gate Types, Exclusive-OR Operator and Gates, High-Impedance Outputs
5. Implementation Technology and Logic Design, Design Concepts and Automation, The Design Space, Design Procedure, The major design steps
6. Programmable Implementation Technologies: Read-Only Memories, Programmable Logic Arrays, Programmable Array Logic, Technology mapping to programmable logic devices
7. Combinational Functions and Circuits
8. Arithmetic Functions and Circuits
9. **Sequential Circuits Storage Elements and Sequential Circuit Analysis**
10. Sequential Circuits, Sequential Circuit Design State Diagrams, State Tables
11. Counters, register cells, buses, & serial operations
12. Sequencing and Control, Datapath and Control, Algorithmic State Machines (ASM)
13. Memory Basics

2

Introduction to Digital Logic

Lecture 9

Sequential Circuits

Storage Elements and Sequential Circuit Analysis

3

Overview


- Storage Elements and Analysis
 - Introduction to sequential circuits
 - Types of sequential circuits
 - Storage elements
 - Latches
 - Flip-flops
 - Sequential circuit analysis
 - State tables
 - State diagrams
 - Circuit and System Timing
- Sequential Circuit Design
 - Specification
 - Assignment of State Codes
 - Implementation

4

Introduction to Sequential Circuits

- A Sequential circuit contains:

 
- Storage elements:
 - Latches or Flip-Flops
- Combinatorial Logic:
 - Implements a multiple-output switching function
 - Inputs are signals from the outside.
 - Outputs are signals to the outside.
 - Other inputs, State or Present State, are signals from storage elements.
 - The remaining outputs, Next State are inputs to storage elements.



5

Introduction to Sequential Circuits

 - Combinatorial Logic
 - Next state function
 $\text{Next State} = f(\text{Inputs, State})$
 - Output function (Mealy)
 $\text{Outputs} = g(\text{Inputs, State})$
 - Output function (Moore)
 $\text{Outputs} = h(\text{State})$
- Output function type depends on specification and affects the design significantly



6

Types of Sequential Circuits

- Depends on the times at which:
 - storage elements observe their inputs, and
 - storage elements change their state

1 Synchronous

- Behavior defined from knowledge of its signals at discrete instances of time
- Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)

2 Asynchronous

- Behavior defined from knowledge of inputs at any instant of time and the order in continuous time in which inputs change
- If clock just regarded as another input, all circuits are asynchronous!

7


Discrete Event Simulation

- In order to understand the time behavior of a sequential circuit we use discrete event simulation.
- Rules:
 - Gates modeled by an ideal (instantaneous) function and a fixed gate delay
 - Any change in input values is evaluated to see if it causes a change in output value
 - Changes in output values are scheduled for the fixed gate delay after the input change
 - At the time for a scheduled output change, the output value is changed along with any inputs it drives

8

Simulated NAND Gate

 - Example: A 2-Input NAND gate with a 0.5 ns. delay:




- Assume A and B have been 1 for a long time
- At time $t=0$, A changes to a 0 at $t=0.8$ ns, back to 1.

t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	A=B=1 for a long time
0	1 \Rightarrow 0	1	1 \Leftarrow 0	0	F(Instantaneous) changes to 1
0.5	0	1	1	1 \Leftarrow 0	F changes to 1 after a 0.5 ns delay
0.8	1 \Leftarrow 0	1	1 \Rightarrow 0	1	F(Instantaneous) changes to 0
0.13	1	1	0	1 \Rightarrow 0	F changes to 0 after a 0.5 ns delay

9

Gate Delay Models

 
- Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:



10

Circuit Delay Model

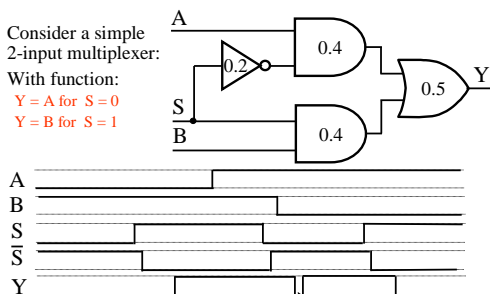- Consider a simple 2-input multiplexer:
- With function:
 - $Y = A$ for $S = 0$
 - $Y = B$ for $S = 1$




- "Glitch" is due to delay of inverter

11

Storing State

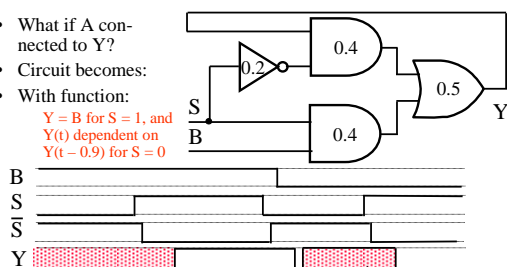- What if A connected to Y?
- Circuit becomes:
- With function:
 - $Y = B$ for $S = 1$, and
 - $Y(t)$ dependent on $Y(t - 0.9)$ for $S = 0$



- The simple combinational circuit has now become a sequential circuit because its output is a function of a time sequence of input signals!

Y is stored value in shaded area

12

Storing State (Continued)

- Simulation example as input signals change with time. Changes occur every 100 ns, so that the tenths of ns delays are negligible.


Time	B	S	Y	Comment
	1	0	0	Y "remembers" 0
	1	1	1	Y = B when S = 1
	1	0	1	Now Y "remembers" B = 1 for S = 0
	0	0	1	No change in Y when B changes
	0	1	0	Y = B when S = 1
	0	0	0	Y "remembers" B = 0 for S = 0
	1	0	0	No change in Y when B changes

- Y represent the state of the circuit, not just an output.

13

Storing State (Continued)

 - Suppose we place an inverter in the "feedback path."



- The following behavior results:

- The circuit is said to be unstable.


- For S = 0, the circuit has become what is called an *oscillator*. Can be used as crude *clock*.

B	S	Y	Comment
0	1	0	Y = B when S = 1
1	1	1	
1	0	1	Now Y "remembers" A
1	0	0	Y, 1.1 ns later
1	0	1	Y, 1.1 ns later
1	0	0	Y, 1.1 ns later

14

Basic (NAND) \bar{S} - \bar{R} Latch

 - "Cross-Coupling" two NAND gates gives the \bar{S} - \bar{R} Latch:



- which has the time sequence behavior:


Time	R	S	Q	Q-bar	Comment
	1	1	?	?	Stored state unknown
	1	0	1	0	"Set" Q to 1
	1	1	1	0	Now Q "remembers" 1
	0	1	0	1	"Reset" Q to 0
	1	1	0	1	Now Q "remembers" 0
	0	0	1	1	Both go high
	1	1	?	?	Unstable!

- S = 0, R = 0 is forbidden as input pattern

15

Basic (NOR) S - R Latch

 
- Cross-coupling two NOR gates gives the S - R Latch:



- Which has the time sequence behavior:

Time	R	S	Q	Q-bar	Comment
	0	0	?	?	Stored state unknown
	0	1	1	0	"Set" Q to 1
	0	0	1	0	Now Q "remembers" 1
	1	0	0	1	"Reset" Q to 0
	0	0	0	1	Now Q "remembers" 0
	1	1	0	0	Both go low
	0	0	?	?	Unstable!


16

 

17

Clocked S - R Latch

 - Adding two NAND gates to the basic \bar{S} - \bar{R} NAND latch gives the clocked S - R latch:



- Has a time sequence behavior similar to the basic S-R latch except that the S and R inputs are only observed when the line C is high.
- C means "control" or "clock".

18

Clocked S - R Latch (continued)

- The Clocked S-R Latch can be described by a table:

S				Q	Q(t)	S	R	Q(t+1)	Comment
C					0	0	0	0	No change
R					0	0	1	0	Clear Q
					0	1	0	1	Set Q
					0	1	1	???	Indeterminate
					1	0	0	1	No change
					1	0	1	0	Clear Q
					1	1	0	1	Set Q
					1	1	1	???	Indeterminate


- The table describes what happens after the clock [at time (t+1)] based on:

- current inputs (S,R) and
- current state Q(t).

19


D Latch

 - Adding an inverter to the S-R Latch, gives the D Latch:
- Note that there are no "indeterminate" states!



The graphic symbol for a D Latch is:

Q	D	Q(t+1)	Comment
0	0	0	No change
0	1	1	Set Q
1	0	0	Clear Q
1	1	1	No Change

 

20

Flip-Flops

- The latch timing problem
- Master-slave flip-flop
- Edge-triggered flip-flop
- Standard symbols for storage elements
- Direct inputs to flip-flops
- Flip-flop timing

21


The Latch Timing Problem

- In a sequential circuit, paths may exist through combinational logic:
 - From one storage element to another
 - From a storage element back to the same storage element
- The combinational logic between a latch output and a latch input may be as simple as an interconnect
- For a clocked D-latch, the output Q depends on the input D whenever the clock input C has value 1

22

The Latch Timing Problem (continued)

- Consider the following circuit:

 

- Suppose that initially Y = 0.



- As long as C = 1, the value of Y continues to change!
- The changes are based on the delay present on the loop through the connection from Y back to Y.
- This behavior is clearly unacceptable.
- Desired behavior: Y changes only once per clock pulse

23


The Latch Timing Problem (continued)

- A solution to the latch timing problem is to break the closed path from Y to Y within the storage element
- The commonly-used, path-breaking solutions replace the clocked D-latch with:
 - a master-slave flip-flop
 - an edge-triggered flip-flop


24

S-R Master-Slave Flip-Flop

- Consists of two clocked S-R latches in series with the clock on the second latch inverted
- The input is observed by the first latch with $C = 1$
- The output is changed by the second latch with $C = 0$
- The path from input to output is broken by the difference in clocking values ($C = 1$ and $C = 0$).
- The behavior demonstrated by the example with D driven by Y given previously is prevented since the clock must change from 1 to 0 before a change in Y based on D can occur.

 

25

 

26

Flip-Flop Problem

- The change in the flip-flop output is delayed by the pulse width which makes the circuit slower or
- S and/or R are permitted to change while $C = 1$
 - Suppose $Q = 0$ and S goes to 1 and then back to 0 with R remaining at 0
 - The master latch sets to 1
 - A 1 is transferred to the slave
 - Suppose $Q = 0$ and S goes to 1 and back to 0 and R goes to 1 and back to 0
 - The master latch sets and then resets
 - A 0 is transferred to the slave
- This behavior is called *1s catching*

27


Flip-Flop Solution

- Use edge-triggering instead of master-slave
- An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a transition of the clock signal
- Edge-triggered flip-flops can be built directly at the electronic circuit level, or
- A master-slave D flip-flop which also exhibits edge-triggered behavior can be used.

28

Edge-Triggered D Flip-Flop


- The edge-triggered D flip-flop is the same as the master-slave D flip-flop
- It can be formed by:
 - Replacing the first clocked S-R latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave S-R flip-flop
- The delay of the S-R master-slave flip-flop can be avoided since the 1s-catching behavior is not present with D replacing S and R inputs
- The change of the D flip-flop output is associated with the negative edge at the end of the pulse
- It is called a *negative-edge triggered* flip-flop

 

29


Positive-Edge Triggered D Flip-Flop

 - Formed by adding inverter to clock input
- Q changes to the value on D applied at the positive clock edge within timing constraints to be specified
- Our choice as the standard flip-flop for most sequential circuits



30


Standard Symbols for Storage Elements

 

31

Direct Inputs


- At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.
- Direct R and/or S inputs that control the state of the latches within the flip-flops are used for this initialization.
- For the example flip-flop shown
 - 0 applied to \bar{R} resets the flip-flop to the 0 state
 - 0 applied to \bar{S} sets the flip-flop to the 1 state

 

32

Flip-Flop Timing Parameters

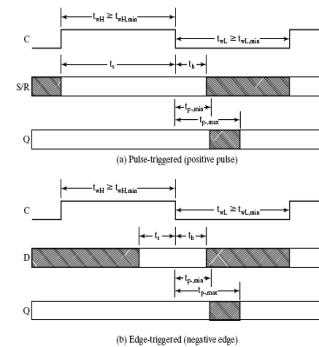- t_s - setup time
- t_h - hold time
- t_w - clock pulse width
- t_{px} - propagation delay
 - t_{PHL} - High-to-Low
 - t_{PLH} - Low-to-High
 - $t_{pd} = \max(t_{PHL}, t_{PLH})$



33


Flip-Flop Timing Parameters (continued)

- t_s - setup time
 - Master-slave - Equal to the width of the triggering pulse
 - Edge-triggered - Equal to a time interval that is generally much less than the width of the triggering pulse
- t_h - hold time - Often equal to zero
- t_{px} - propagation delay
 - Same parameters as for gates except
 - Measured from clock edge that triggers the output change to the output change

34

Sequential Circuit Analysis

 
- General Model
 - Current State at time (t) is stored in an array of flip-flops.
 - Next State at time (t+1) is a Boolean function of State and Inputs.
 - Outputs at time (t) are a Boolean function of State (t) and (sometimes) Inputs (t).



35

 Example 1

- Input: $x(t)$
- Output: $y(t)$
- State: $(A(t), B(t))$
- What is the Output Function?
- What is the Next State Function?



36


Example 1 (continued)

- Boolean equations for the functions:

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \bar{A}(t)x(t)$$


$$y(t) = \bar{x}(t)(B(t) + A(t))$$

 

37

 Example 1 (continued)

- Where in time are inputs, outputs and states defined?



38

State Table Characteristics

- State table – a multiple variable table with the following four sections:
 - Present State – the values of the state variables for each allowed state.
 - Input – the input combinations allowed.
 - Next-state – the value of the state at time (t+1) based on the present state and the input.
 - Output – the value of the output as a function of the present state and (sometimes) the input.
- From the viewpoint of a truth table:
 - the inputs are Input, Present State
 - and the outputs are Output, Next State

39

Example 1: State Table

- The state table can be filled in using the next state and output equations:
- $A(t+1) = A(t)x(t) + B(t)x(t)$
- $B(t+1) = \bar{A}(t)x(t)$
- $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

40

Example 1: Alternate State Table

- 2-dimensional table that matches well to a K-map. Present state rows and input columns in Gray code order.
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$
 - $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State	Next State		Output	
	x(t)=0	x(t)=1	x(t)=0	x(t)=1
A(t) B(t)	A(t+1)B(t+1)	A(t+1)B(t+1)	y(t)	y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

41

State Diagrams

- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - A circle with the state name in it for each state
 - A directed arc from the Present State to the Next State for each state transition
 - A label on each directed arc with the Input values which causes the state transition, and
 - A label:
 - On each circle with the output value produced, or
 - On each directed arc with the output value produced.

42


State Diagrams

- Label form:
 - On circle with output included:
 - state/output
 - Moore type output depends only on state
 - On directed arc with the output included:
 - input/output
 - Mealy type output depends on state and input

43

 Example 1: State Diagram

- Which type?
- Diagram gets confusing for large circuits
- For small circuits, usually easier to understand than the state table



44


Moore and Mealy Models

- Sequential Circuits or Sequential Machines are also called *Finite State Machines* (FSMs). Two formal models exist:
 - Moore Model**
 - Named after E.F. Moore.
 - Outputs are a function of ONLY of states
 - Usually specified on the states.
 - Mealy Model**
 - Named after G. Mealy
 - Outputs are a function of inputs AND states
 - Usually specified on the state transition arcs.
- In contemporary design, models are sometimes mixed Moore and Mealy


45

Moore and Mealy Example Diagrams

 - Mealy Model State Diagram maps inputs and state to outputs



 - Moore Model State Diagram maps states to outputs



46

Moore and Mealy Example Tables

- Mealy Model state table maps inputs and state to outputs

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1


- Moore Model state table maps state to outputs

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

47

Example 2: Sequential Circuit Analysis

- Logic Diagram:

 

48

Example 2: Flip-Flop Input Equations

- Variables


- Inputs: None
- Outputs: Z
- State Variables: A, B, C

- Initialization:

- Reset to (0,0,0)

- Equations

$$\begin{aligned} A(t+1) &= B(t)C(t) & Z &= B(t)C(t) \\ B(t+1) &= \overline{B}(t)C(t) + B(t)\overline{C}(t) \\ C(t+1) &= \overline{A}(t)\overline{C}(t) \end{aligned}$$

 


Example 2: State Table

$$X' = X(t+1)$$

$$\begin{aligned} A(t+1) &= B(t)C(t) \\ B(t+1) &= \overline{B}(t)C(t) + B(t)\overline{C}(t) \\ C(t+1) &= \overline{A}(t)\overline{C}(t) \end{aligned}$$

A	B	C	A'B'C'	Z
0	0	0	0 0 1	0
0	0	1	0 1 0	0
0	1	0	0 1 1	0
0	1	1	1 0 0	1
1	0	0	0 0 0	0
1	0	1	0 1 0	0
1	1	0	0 1 0	0
1	1	1	1 0 0	1


Example 2: State Diagram

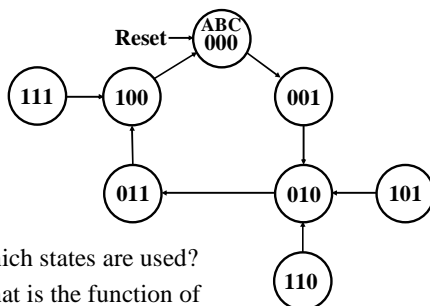

- Which states are used?
- What is the function of the circuit?


Circuit and System Level Timing

 - Consider a system comprised of ranks of flip-flops connected by logic:
- If the clock period is too short, some data changes will not propagate through the circuit to flip-flop inputs before the setup time interval begins



Circuit and System Level Timing (continued)

 - Timing components along a path from flip-flop to flip-flop



Circuit and System Level Timing (continued)

- New Timing Components
 - t_p - clock period - The interval between occurrences of a specific clock edge in a periodic clock
 - $t_{pd,COMB}$ - total delay of combinational logic along the path from flip-flop output to flip-flop input
 - t_{slack} - extra time in the clock period in addition to the sum of the delays and setup time on a path
 - Can be either positive or negative
 - Must be greater than or equal to zero on all paths for correct operation

Circuit and System Level Timing (continued)

- Timing Equations

$$t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

– For t_{slack} greater than or equal to zero,

$$t_p \geq \max(t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

for all paths from flip-flop output to flip-flop input

- Can be calculated more precisely by using t_{PHL} and t_{PLH} values instead of t_{pd} values, but requires consideration of inversions on paths

55

Calculation of Allowable $t_{\text{pd,COMB}}$

- Compare the allowable combinational delay for a specific circuit:

a) Using edge-triggered flip-flops

b) Using master-slave flip-flops

- Parameters

– $t_{\text{pd,FF}}(\text{max}) = 1.0 \text{ ns}$

– $t_s(\text{max}) = 0.3 \text{ ns}$ for edge-triggered flip-flops

– $t_s = t_{\text{wH}} = 1.0 \text{ ns}$ for master-slave flip-flops

– Clock frequency = 250 MHz

56

Calculation of Allowable $t_{\text{pd,COMB}}$ (continued)

- Calculations: $t_p = 1/\text{clock frequency} = 4.0 \text{ ns}$

– Edge-triggered: $4.0 \geq 1.0 + t_{\text{pd,COMB}} + 0.3$, $t_{\text{pd,COMB}} \leq 2.7 \text{ ns}$

– Master-slave: $4.0 \geq 1.0 + t_{\text{pd,COMB}} + 1.0$, $t_{\text{pd,COMB}} \leq 2.0 \text{ ns}$

- Comparison: Suppose that for a gate, average $t_{\text{pd}} = 0.3 \text{ ns}$

– Edge-triggered: Approximately 9 gates allowed on a path

– Master-slave: Approximately 6 to 7 gates allowed on a path

57